



King Saud University


College of Computer and Information Sciences

Department of Computer Science


CSC 220: Computer Organization

Tutorial 11: Datapath Design

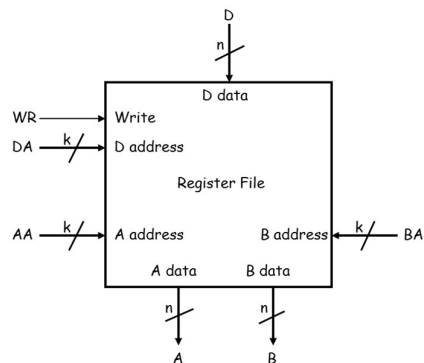Q1: Show how to construct a $4 \times n$ register file using necessary registers, MUX and decoder.




Solution:

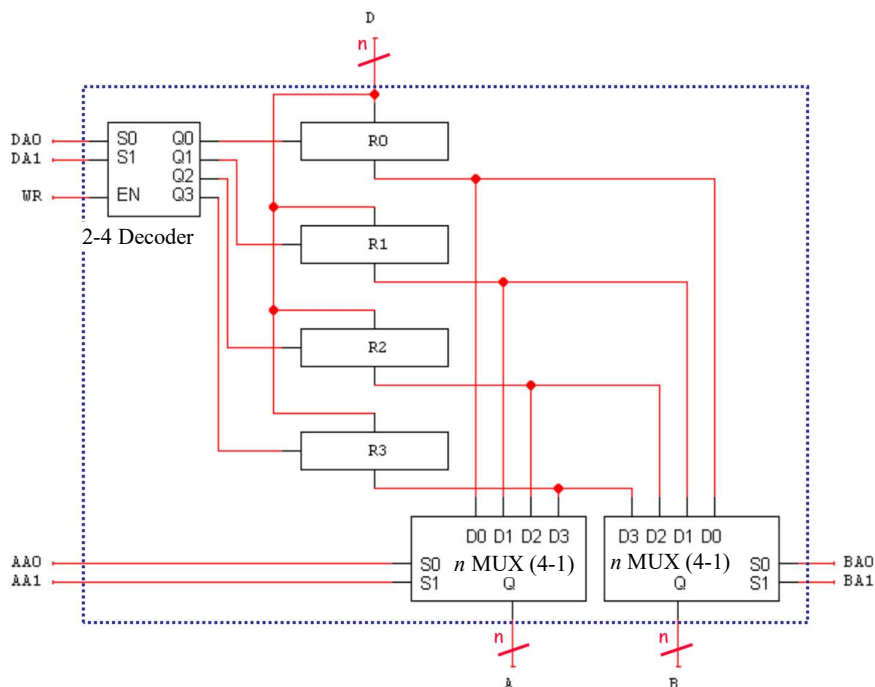


Q2: Show the block diagram representation of a general datapath using the block diagram for a register file ($2^m \times n$) and the function unit.

Solution:

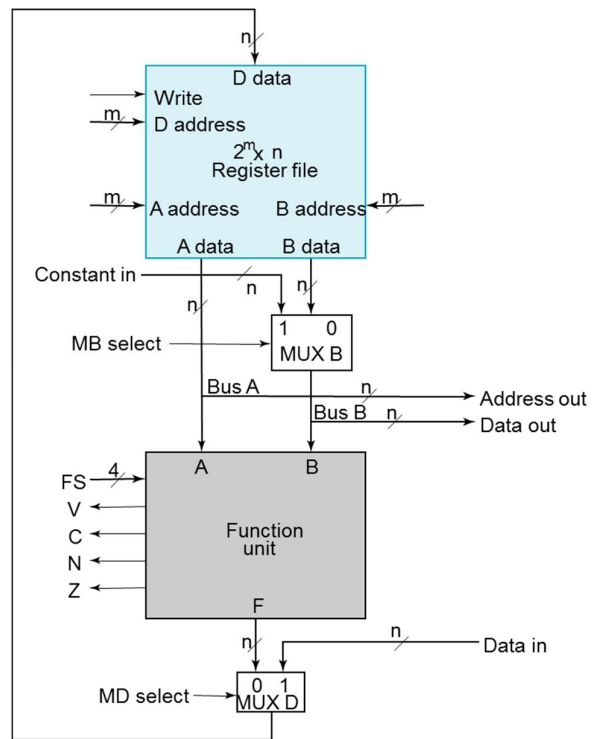

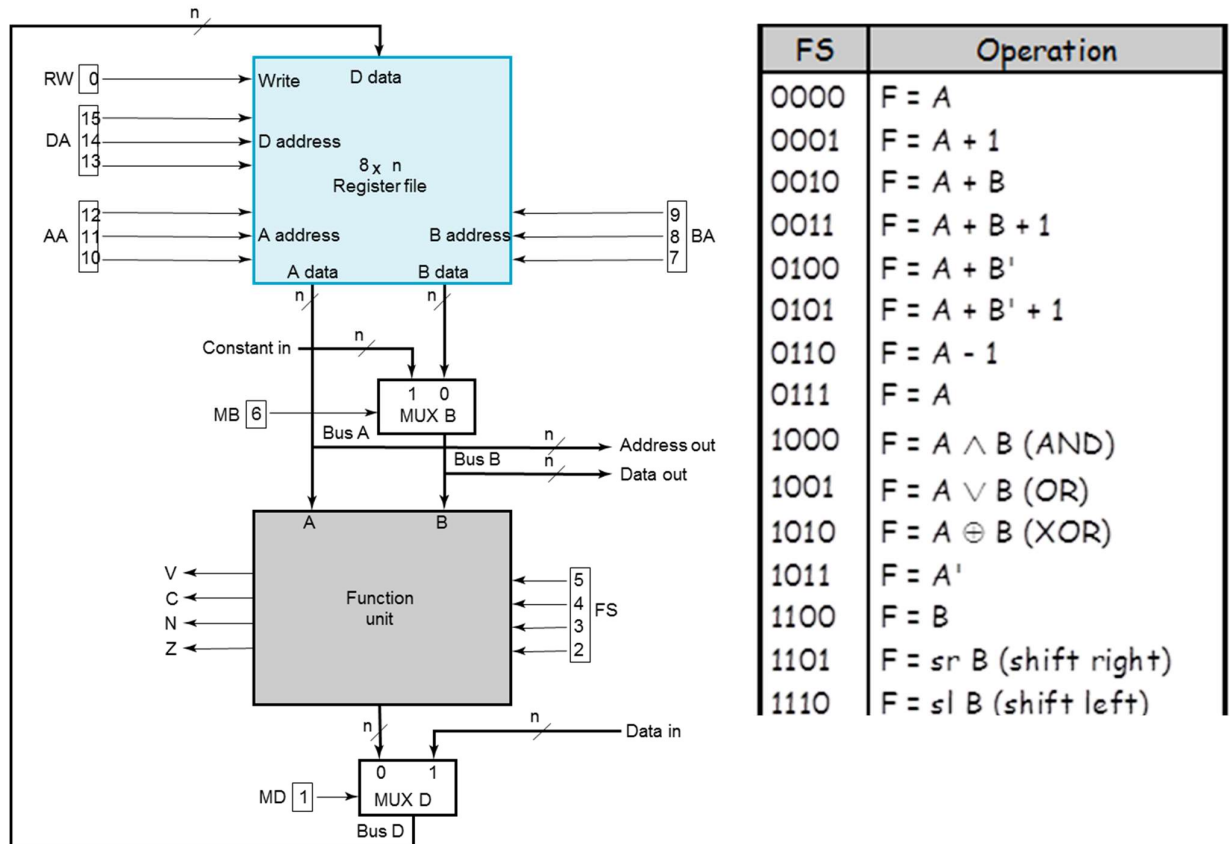Q 3:

Consider the following datapath and function table.



Show the 16 bit control words on the table below to perform the following microoperations assuming that the registers are of 8 bits


Microoperations	DA (15-13)	AA (12-10)	BA (9-7)	MB (6)	FS (5-2)	MD (1)	RW (0)
$R1 \leftarrow R1 - 5$	001	001	xxx	1	0101	0	1
$R0 \leftarrow R1 + R5$	000	001	101	0	0010	0	1
$R7 \leftarrow R7 + 1$	111	111	xxx	x	0001	0	1
$R4 \leftarrow sl\ R6$	100	xxx	110	0	1110	0	1
$M[R3] \leftarrow R1$	xxx	011	001	0	xxxx	x	0

Question 4:

Here is the most basic datapath you have studied.

– The ALU's two data inputs.

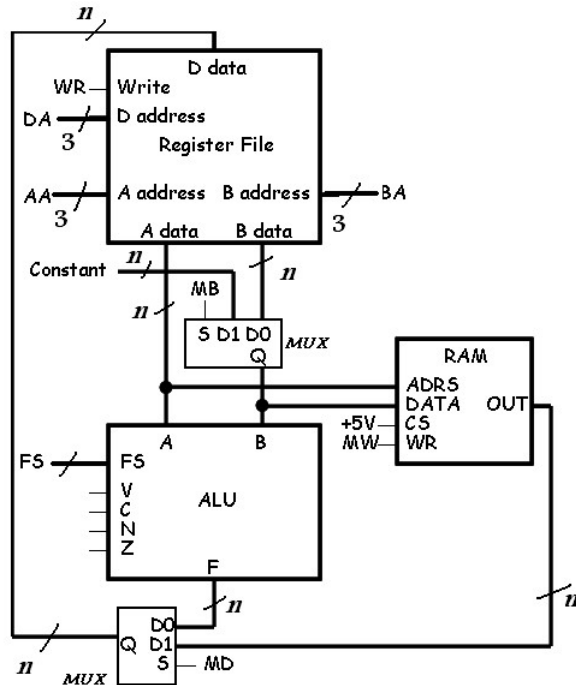– The ALU computes a result, which is saved back to the registers. AA, BA, DA, WR, MB, MD, MW, and FS are control signals. Their values determine the exact actions taken by the datapath, and which registers are used and for what operation.



FS	Operation
0000	$F = A$
0001	$F = A + 1$
0010	$F = A + B$
0011	$F = A + B + 1$
0100	$F = A + B'$
0101	$F = A + B' + 1$
0110	$F = A - 1$
0111	$F = A$
1000	$F = A \wedge B$ (AND)
1001	$F = A \vee B$ (OR)
1010	$F = A \oplus B$ (XOR)
1100	$F = B$
1011	$F = A'$

– **Fill in the required information** in the answer table to perform the following instructions assuming that the registers of 8 bits, and their initial signed 2's complement values were, $R0 = 0E$, $R1 = 0F$, $R2 = 09$, $R3 = 0B$, data in memory as shown, and the initial values of V, C, N, Z were 0's. The required information are:

- The generated control signals (**AA, BA, DA, WR, MB, MD, MW, FS**) on the diagram to perform the instruction.
- The values of **V, C, N, and Z status flags** after each instruction.
- The **contents of memory and registers** after executing the 5 instructions.

$R0 \leftarrow M[R3]$
 $R3 \leftarrow M[R2]$
 $R1 \leftarrow R0 + 0F$
 $M[R2] \leftarrow R1$
 $M[R1] \leftarrow R3$

address	memory
09	20
0A	A3
0B	21
2E	34
2F	E4
30	71

Answer

AA	BA	DA	WR	MB	MD	MW	FS	V	C	N	Z	Microoperations
011	XXX	000	1	X	1	0	XXXX	■	■	■	■	$R0 \leftarrow M[R3]$
								■	■	■	■	$R3 \leftarrow M[R2]$
												$R1 \leftarrow R0 + 0F$
								■	■	■	■	$M[R2] \leftarrow R1$

