



**King Saud University**  
College of Computer and Information Sciences  
Department of Computer Science

**CSC 220: Computer Organization**

**Labwork-1**

1. Introduction of logisim software
2. How to draw AND, OR and Not Gate
3. Test the above gates and draw truth table

Demo

<https://www.youtube.com/watch?v=dYZ-Hwbcnq4>