



**King Saud University**  
**College of Computer and Information Sciences**  
**Department of Computer Science**  
**CSC 220: Computer Organization**

**Tutorial 6: MUX, DeMUX, Encoder, Decoder**

1. Multiplexer
  - a. What is a multiplexer? Give the abbreviated truth table of a  $4 \times 1$  multiplexer.
  - b. Design the circuit with basic logic gates.
  - c. Implement the following Boolean function with a multiplexer:  
 $F(A, B, C, D) = \sum m(0, 1, 3, 4, 8, 9, 15)$
2. Implement four-bit even parity generator using a demultiplexer 1-16
3. Designing a decoder
  - a. Give the truth table for a 2-to-4 decoder with enable
  - b. Design the circuit.
4. Construct a 4-to-16-line decoder with five 2-to-4 line decoders with enable.
5. Design a decimal to BCD **encoder**.

**Home Works**

**Text book problems: 3-28 to 3-30, 3-44, 3-46, 3-47**

**Additional Problems**

1. Implement the following function using a multiplexer 8/1  
 $F(x,y,z) = xy'z + x'y'z + xyz$
2. Implement the following Boolean function with a decoder.  
 $F(A, B, C, D) = \sum m(0, 1, 3, 4, 8, 9, 15)$