




Labwork - 8

1. Introduction

we will learnt how to use clock, register, splitter and more tools to design the bus.

2. Experiments

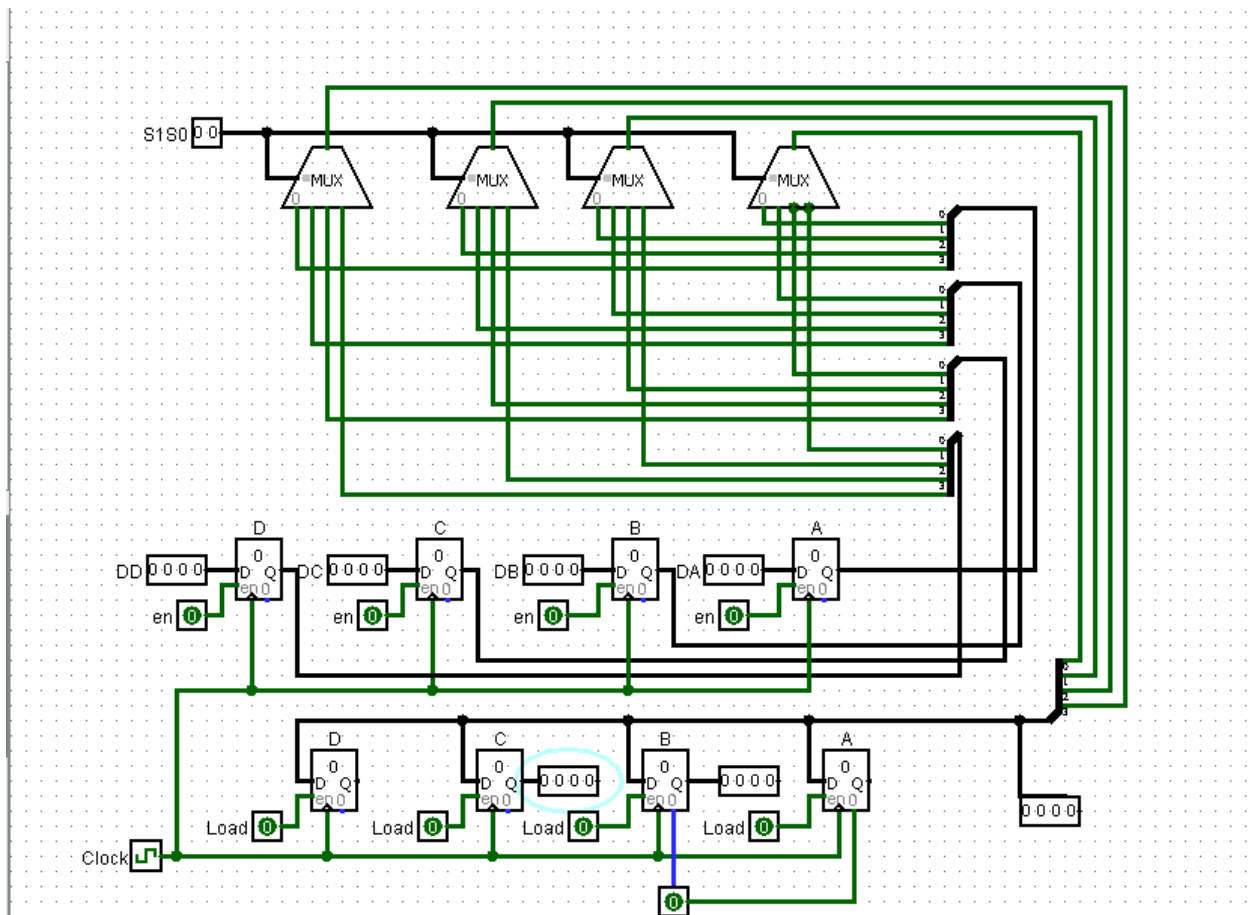

3. Results

No Results.

4. Discussion

we learned how the bus goes on. We use four multiplexer and four register which are connected in a specific links contains splitters. Then connected with a clock.