



CSC 220: Computer Organization

Unit 5

COMBINATIONAL CIRCUITS-1

Prepared by:

Md Saiful Islam, PhD

Department of Computer Science

College of Computer and Information Sciences


Overview

- Introduction to Combinational Circuits
- Adder
- Ripple Carry Adder
- Subtraction
- Adder/Subtractor

Chapter-3

M. Morris Mano, Charles R. Kime and Tom Martin, **Logic and Computer Design Fundamentals**, Global (5th) Edition, Pearson Education Limited, 2016. ISBN: 9781292096124


Combinational circuits

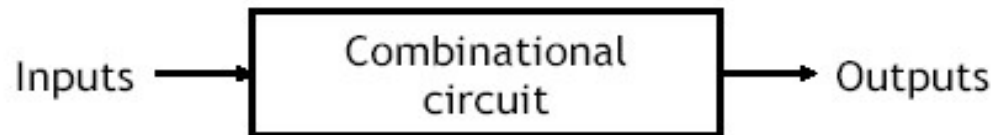

- So far we've only worked with **combinational circuits**, where applying the same inputs always produces the same outputs.
 - This corresponds to a mathematical function, where every input has a single, unique output.
 - In programming terminology, combinational circuits are similar to "functional programs" that do not contain variables and assignments.
- Such circuits are comparatively easy to design and analyze.

Binary addition by hand

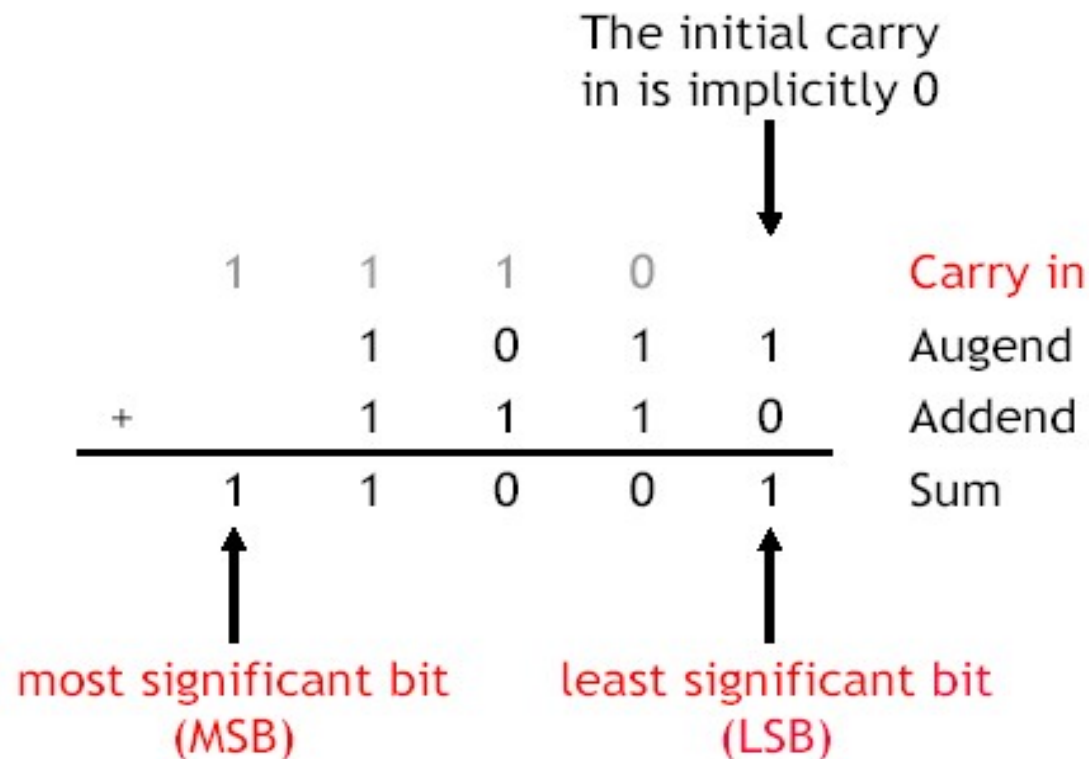- You can add two binary numbers one column at a time starting from the right, just like you add two decimal numbers.
- But remember it's binary. For example, $1 + 1 = 10$ and you have to carry!



Adder

- Design an Adder for 1-bit numbers?
- **1. Specification:**
 - 2 inputs (X,Y)
 - 2 outputs (C,S)

Adder ...


- Design an Adder for 1-bit numbers?
- **1. Specification:**
2 inputs (X,Y)
2 outputs (C,S)
- **2. Formulation:**

X	Y	C	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

Adder ...

- Design an Adder for 1-bit numbers?
- **1. Specification:**
2 inputs (X,Y)
2 outputs (C,S)
- **2. Formulation:**
- **3. Optimization/Circuit**


X	Y	C	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

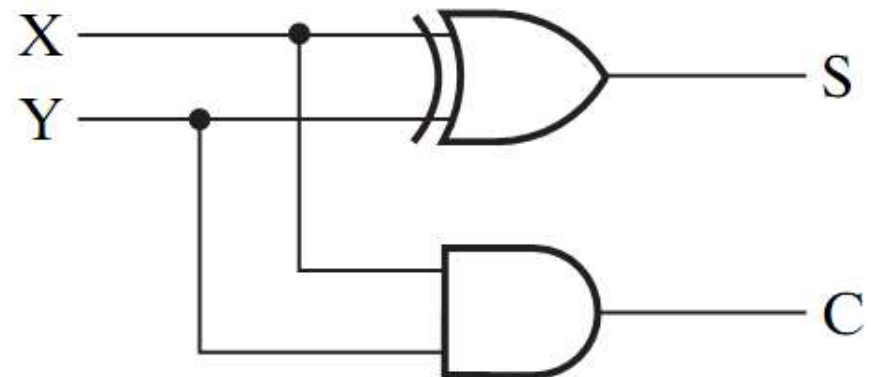

Half Adder ...

- This adder is called a Half Adder
- **Q: Why?**

X	Y	C	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

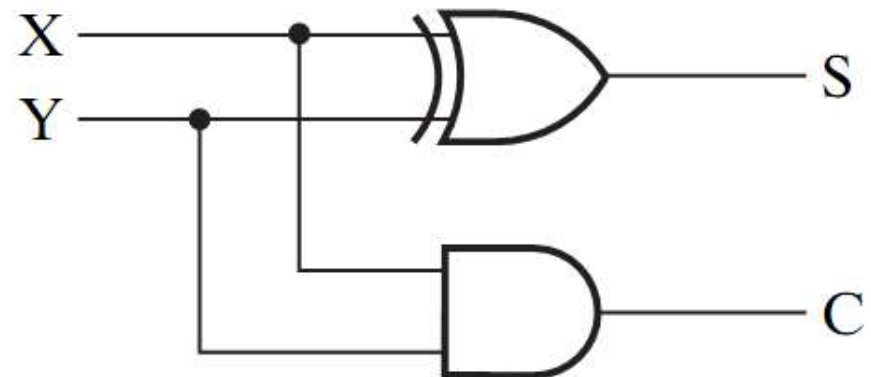

Full Adder

- A combinational circuit that adds 3 input bits to generate a Sum bit and a Carry bit
- A truth table and sum of minterm equations for C and S are shown below.

	X	Y	Z	C	S
	0	0	0	0	0
	0	0	1	0	1
	0	1	0	0	1
$0 + 1 + 1 = 10$ →	0	1	1	1	0
	1	0	0	0	1
	1	0	1	1	0
	1	1	0	1	0
$1 + 1 + 1 = 11$ →	1	1	1	1	1

$$C(X,Y,Z) = \sum m(3,5,6,7)$$

$$S(X,Y,Z) = \sum m(1,2,4,7)$$

Full Adder

- A combinational circuit that adds 3 input bits to generate a Sum bit and a Carry bit

X	Y	Z	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Sum

X \ YZ	00	01	11	10
0	0	1	0	1
1	1	0	1	0

$$\begin{aligned}
 S &= X'Y'Z + X'YZ' \\
 &+ XY'Z' + XYZ \\
 &= X \oplus Y \oplus Z
 \end{aligned}$$

Carry

X \ YZ	00	01	11	10
0	0	0	1	0
1	0	1	1	1

$$C = XY + YZ + XZ$$

Full Adder

Full Adder = 2 Half Adders

Manipulating the Equations:

$$S = (X \oplus Y) \oplus Z$$

$$C = XY + XZ + YZ$$

$$= XY + XZ(Y + Y') + YZ(X + X')$$

$$= XY + XYZ + XY'Z + X'YZ + \cancel{XYZ}$$

$$= XY(1 + Z) + Z(XY' + X'Y)$$

$$= XY + Z(X \oplus Y)$$


Full Adder

Full Adder = 2 Half Adders

Manipulating the Equations:

$$S = (X \oplus Y) \oplus Z$$
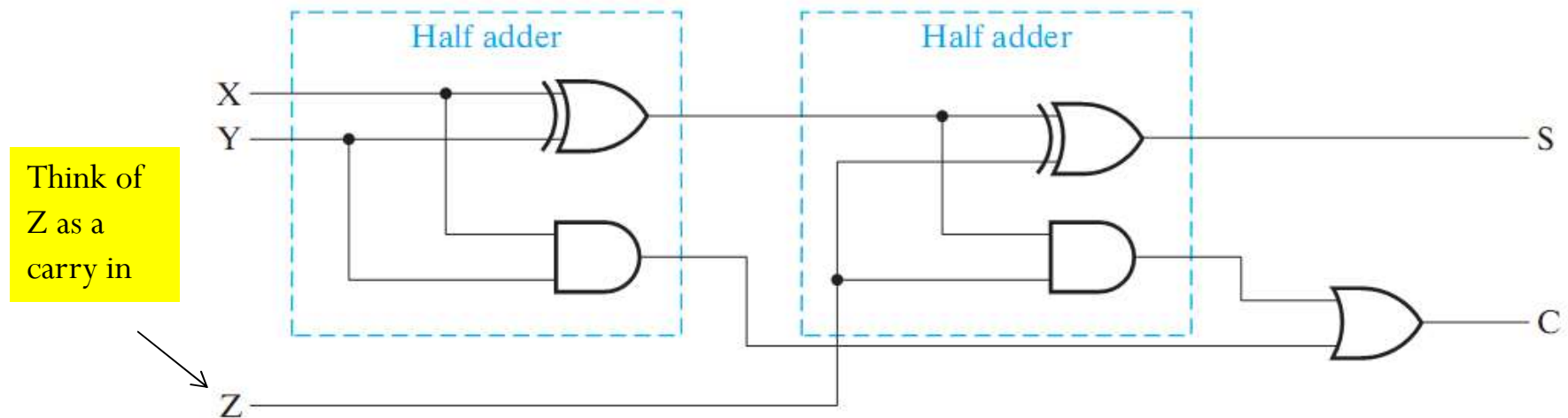
$$C = XY + XZ + YZ = XY + Z(X \oplus Y)$$



Src: Mano's Book

n-bit Adder

- How to build an adder for n-bit numbers?
 - Example: 4-Bit Adder
 - Inputs ?
 - Outputs ?
 - What is the size of the truth table?
 - How many functions to optimize?

n-bit Adder ...

- How to build an adder for n-bit numbers?
 - Example: 4-Bit Adder
 - Inputs ? 9 inputs
 - Outputs ? 5 outputs
 - What is the size of the truth table? 512 rows!
 - How many functions to optimize? 5 functions

Binary Parallel Adder


- To add n-bit numbers:
- Use n Full-Adders in parallel
- The carries propagates as in addition by hand
- Use Z in the circuit as a C_{in}

Example

```
  0 1 0 0 0
    0 1 0 1
  0 1 1 0
  1 0 1 1
```

Binary Parallel Adder ..

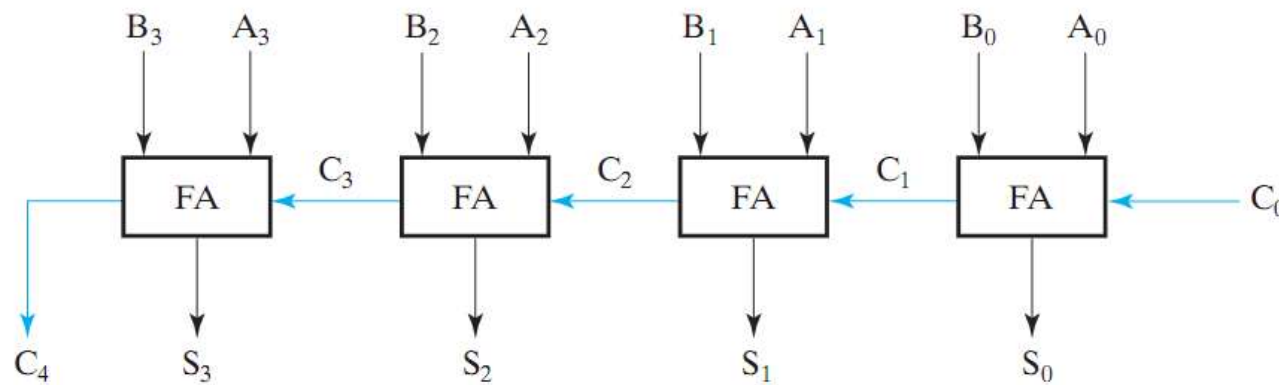- To add n-bit numbers:
- Use n Full-Adders in parallel
- The carries propagates as in addition by hand



C	0	1	0	0	0
A	0	1	0	1	
B	0	1	1	0	
S	1	0	1	1	

This adder is called *ripple carry adder*


Src: Mano's Book

Subtraction (2's Complement)

- How to build a subtractor using 2's complement?

$$S = A - B$$

$$= A + (-B)$$

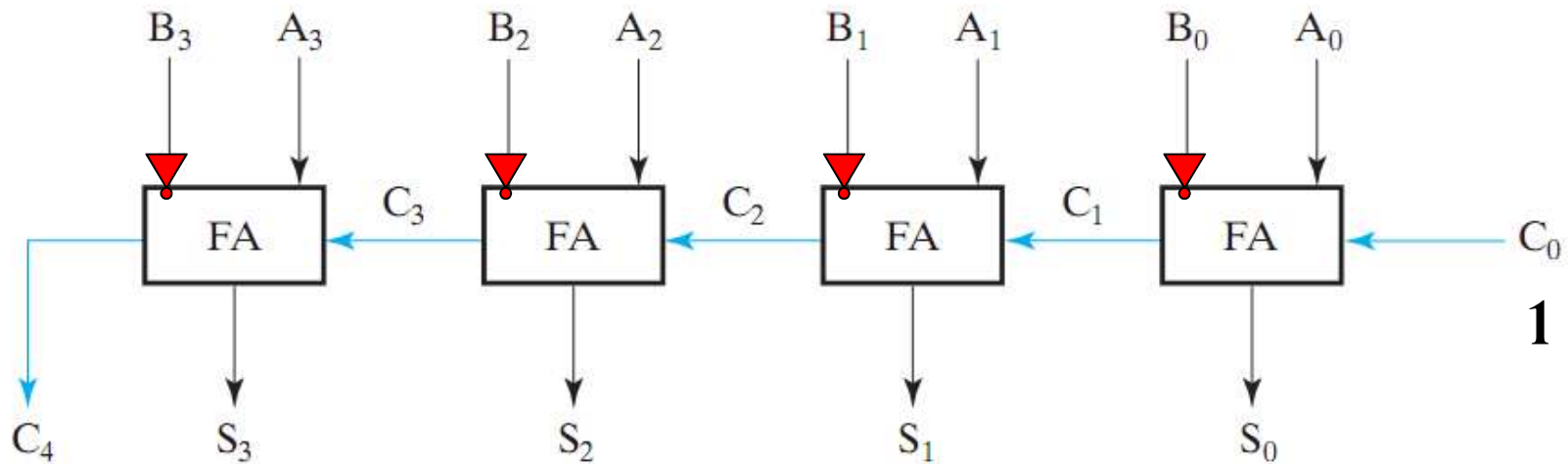

A 0 1 0 1
 B 0 1 1 0


C 0 0 0 0 0

A 0 1 0 1
 -B 1 0 1 0
 S 1 1 1 1

Src: Mano's Book

Adder-Subtractor

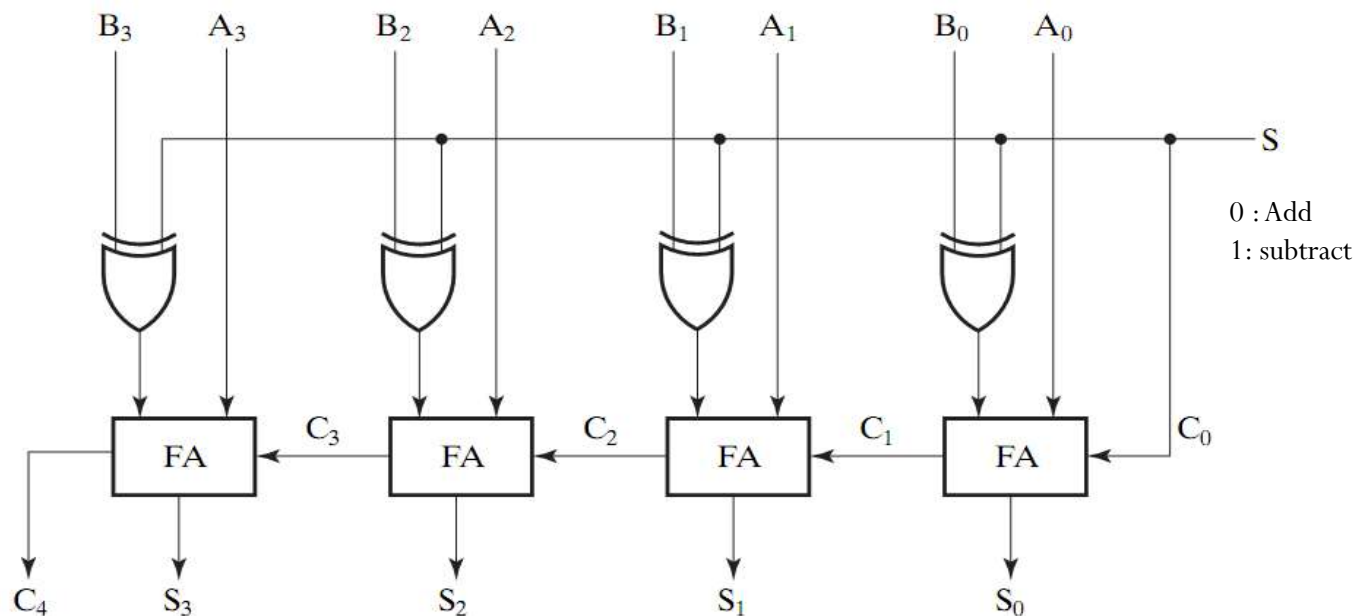- How to build a circuit that performs both addition and subtraction?




C	0	1	0	0	0
A	0	1	0	1	
B	0	1	1	0	
S	1	0	1	1	

Src: Mano's Book

Using full adders and XOR we can build an Adder/Subtractor!

Carry Look Ahead Adder

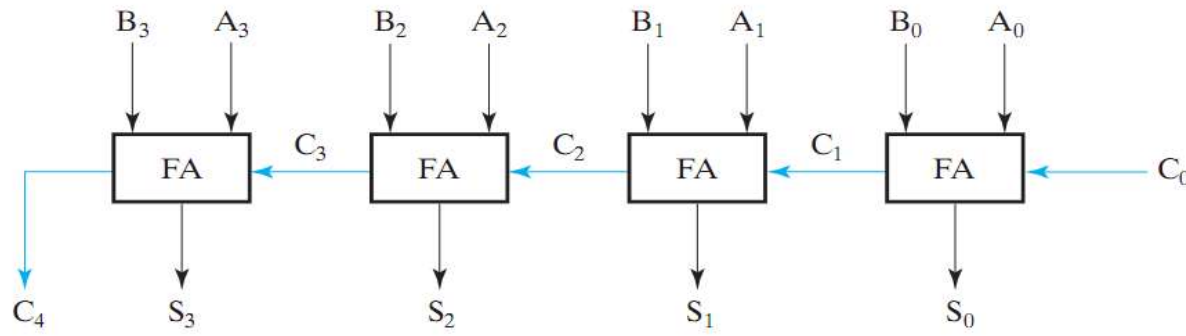

- How to reduce propagation delay of ripple carry adders?
- **Carry look ahead adder:** All carries are computed as a function of C_0 (independent of n !)
- It works on the following standard principles:
 - A carry bit is generated when both input bits A_i and B_i are 1, or
 - When one of input bits is 1, and a carry in bit exists

Carry bits \longrightarrow $C_n \ C_{n-1} \dots C_i \dots C_2 \ C_1 \ C_0$
 $A_{n-1} \dots A_i \dots A_2 \ A_1 \ A_0$
 $B_{n-1} \dots B_i \dots B_2 \ B_1 \ B_0$

Carry Out \longrightarrow $S_n \ S_{n-1} \dots S_i \dots S_2 \ S_1 \ S_0$

Detecting signed overflow

- The easiest way to detect signed overflow is to look at all the sign bits.

$$\begin{array}{r} \textcircled{0}100 \quad (+4) \\ + \quad \textcircled{0}101 \quad + (+5) \\ \hline 0\textcircled{1}001 \quad (-7) \end{array}$$


$$\begin{array}{r} \textcircled{1}100 \quad (-4) \\ + \quad \textcircled{1}011 \quad + (-5) \\ \hline 1\textcircled{0}111 \quad (+7) \end{array}$$

- Overflow occurs only in the two situations above.
 - If you add two *positive* numbers and get a *negative* result.
 - If you add two *negative* numbers and get a *positive* result.
- Overflow can never occur when you add a positive number to a negative number. (Do you see why?)




Overflow


Example1:


$$\begin{array}{r} 0110101_2 \quad (= 53_{10}) \\ + 0101010_2 \quad (= 42_{10}) \\ \hline 1011111_2 \quad (= -33_{10}) \end{array}$$


Example2:


$$\begin{array}{r} 1010101_2 \quad (= -43_{10}) \\ + 1001010_2 \quad (= -54_{10}) \\ \hline 0011111_2 \quad (= 31_{10}) \end{array}$$

Example3:


$$\begin{array}{r} 0110101_2 \quad (= 53_{10}) \\ + 1101010_2 \quad (= -22_{10}) \\ \hline 0011111_2 \quad (= 31_{10}) \end{array}$$

Example4:


$$\begin{array}{r} 0010101_2 \quad (= 21_{10}) \\ + 0101010_2 \quad (= 42_{10}) \\ \hline 0111111_2 \quad (= 63_{10}) \end{array}$$

Detecting Sign Overflow ...

