



Tutorial 7: Flip Flop



Q1:

- Give the transition table and Represent the synchronous SR Flip Flop with NAND gates.
- Explain the role of the control signal in the function of SR Flip Flop
- Explain how to obtain D Flip Flop from the SR structure.


Q2:

- Give the transition table of JK Flip Flop.
- Show how to implement a JK flip-flop using NAND gates
- Explain how to obtain T Flip Flop from the JK structure.

  
Q3: For the given diagram below- what will be the output waveform at Q and Y (assuming that initially Q = 0)?



 
Q4: Determine the output frequency (f_{out}) for a frequency division circuit that contains 2 flip-flops with an input clock frequency of 20.48 MHz.



Q5: Consider the following JK Flip Flop.

 

 - Explain the role of the direct inputs (PS and PR) with characteristic table.
- Represent the outputs of the JK Flip flop (s) for the following input signal waves .



Home Works

Text book problems: 4-4, 4-5 (a-b), 4-6(a-b)

Additional Problems

1. Determine the output frequency for a frequency division circuit that contains 12 flip-flops with an input clock frequency of 20.48 MHz.

- a. 10.24 kHz, b. 5 kHz, c. 30.24 kHz, d. 15 kHz

2. Clock speed is measured in

- (a) bits per second (b) baud (c) bytes (d) Hertz

3. Explain how would draw the Y and Z activity in the following problem (if we ignore propagation delay and assume Y and Z start at 0)?

