

Question 1. Short Questions (8 Marks: 8×1)

- i. Extend the sign of the 4-bit 2's complement binary number 1011 to convert it into a 8-bit number.

Ans. 11111011


- ii. What are the disadvantages of 1's complement representation of binary number?

Ans. Two representation for 0 (+0= 0000 , -0 = 1111)

- iii. How many full adders are required to design a 32-bit parallel adder?

Ans. 32 full adder

 - iv. Give the truth table for a 1-to-4 demultiplexer.



- v. A digital computer has a common bus system for 64 registers of 16 bits each. The bus is constructed with multiplexers. How many multiplexers are needed? How many selection bits are required?

Ans. 16 multiplexer

6 selection bits required

vi. Give the transition table of J-K Flip Flop.

Clk	J	K	Q(t+1)
0	X	X	No change Q(t)
1	0	0	No Change Q(t)
1	0	1	0
1	1	0	1
1	1	1	Q'(t)

vii. Write RTL instructions for the following operations: write the data contained in register R3 to the memory location contained in register AR.

Ans. $M[AR] \leftarrow R3$

viii. If a register containing data (11001100) is subjected to arithmetic shift right operation, then the content of the register after the operation.

Ans. 11100110

Question 2. Short Questions (8 Marks: 2+2+2+2)


i. Suppose we have 1024 x 16 RAM chips. How many chips are needed to provide a memory capacity of 16KB? What will be the size of address bus for the 16 KB RAM?

Number of chips	Size of address bus
8	13

ii. Assuming registers are 8-bits width, and R1 = BE, R2 = 6D, R3 = 9F, R4 = FF, where numbers are represented in HEX and in 2's complement. If the instruction $R3 \leftarrow R1 - R2$ is executed? (**Show the steps of computation**). What is the content of R3 in Hex and what are the value of flags overflow "V", zero "Z", carry "C", and negative "N"?

R3	V	Z	C	N
51	1	0	1	0

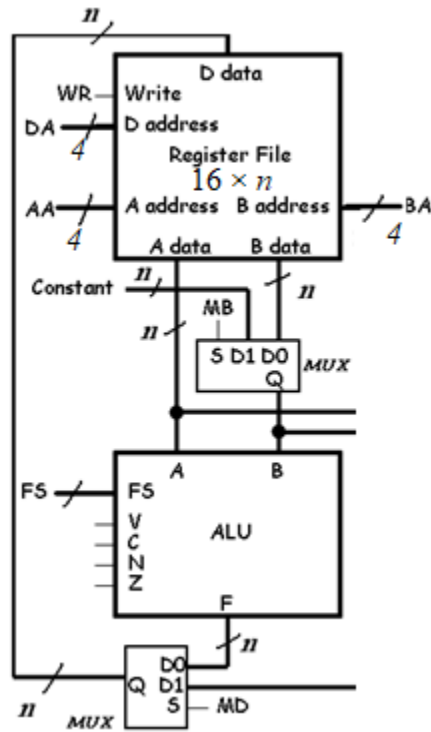- iii. Give the block diagram of a datapath, that contains a register file ($16 \times n$) and a function unit, showing all the control signals.



- iv. Write the instruction format for
a) **Register type instructions**


15	9	8	6	5	3	2	0
Opcode				Destination register (DR)	Source register A (SA)	Source register B (SB)	

- b) **Jump and branch type instructions**


15	9	8	6	5	3	2	0
Opcode				Address (AD) (Left)	Source register A (SA)	Address (AD) (Right)	

Question 3 (6 Marks: 2+2+2)

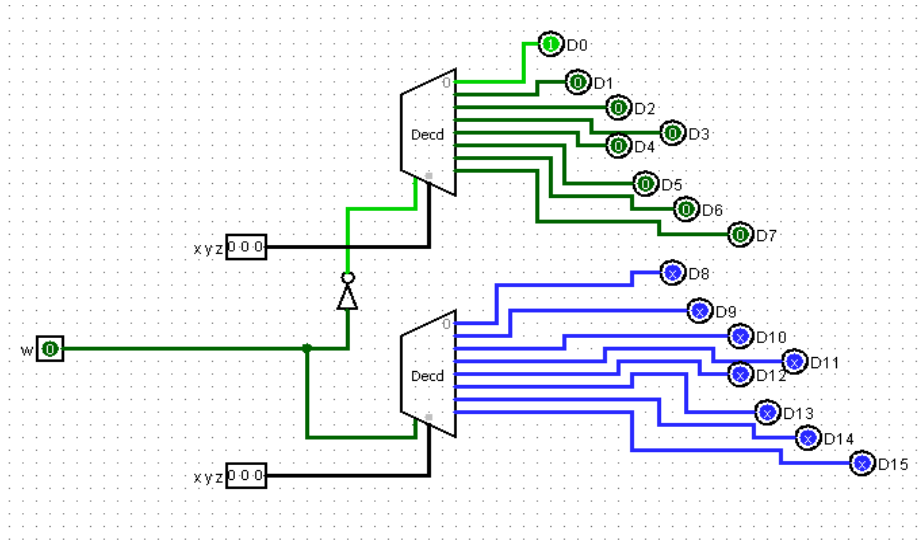- (a) Construct a **4x16** decoder from **two 3x8** decoders with 1-enable.




 (b) For the given diagram below, what will be the output waveform at Q and Y (assuming that initially Q = 0)?



(c) Determine the output frequency (f_{out}) for a frequency division circuit that contains 3 flip-flops with an input clock frequency of 24.48 MHz


	Output Frequency
--	------------------

 

3.6 MHz


Question 4 (6 Marks: 4+2)

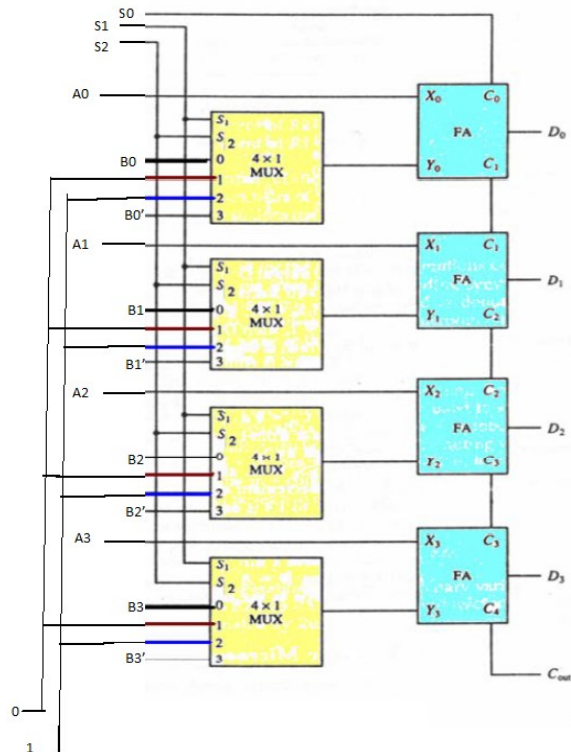- (a) Consider the following arithmetic unit. Write the function Y and D in terms of A and B for each of the three bit selections.



S2	S1	S0	Y =	D =
0	0	0	B	D= A+B
0	0	1	B	D= A+B+1
0	1	0	0	D= A
0	1	1	0	D= A+1
1	0	0	1111(-1)	D= A-1
1	0	1	1111(-1)	D= A
1	1	0	B'	D= A+B'
1	1	1	B'	D= A+B'+1 = A-B

 (b) Construct an asynchronous BCD counter.



Question 5 (6 Marks: 3+2+1)

Consider the datapath below described by table 8.5.

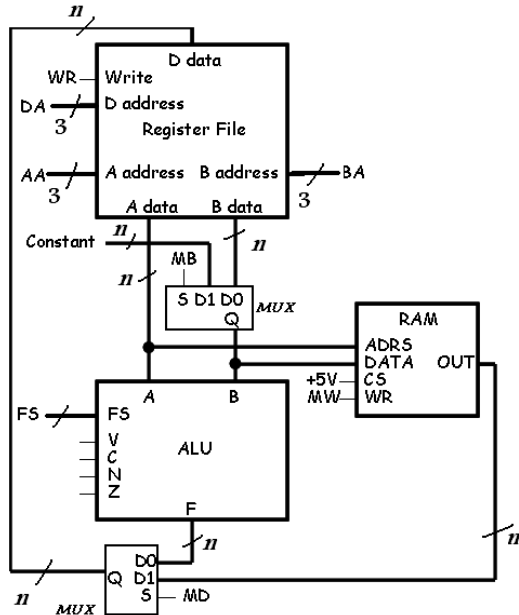


TABLE 8-5
Encoding of Control Word for the Datapath

DA, AA, BA		MB	FS	MD	RW
Function Code	Function Code	Function	Code	Function Code	Function Code
R0	000	Register 0	$F = A$	0000	Function 0
R1	001	Constant 1	$F = A + 1$	0001	Data in 1
R2	010		$F = A + B$	0010	Write 1
R3	011		$F = A + B + 1$	0011	
R4	100		$F = A + \overline{B}$	0100	
R5	101		$F = A + \overline{B} + 1$	0101	
R6	110		$F = A - 1$	0110	
R7	111		$F = A$	0111	
			$F = A \wedge B$	1000	
			$F = A \vee B$	1001	
			$F = A \oplus B$	1010	
			$F = \overline{A}$	1011	
			$F = B$	1100	
			$F = sr B$	1101	
			$F = sl B$	1110	

Fill the required information in the table below to perform the following instructions assuming that the registers are of 8 bits, and their initial signed 2's complement values (in HEX) were, R0= 0E, R1 = 09, R2 = 2E, R3 = 2F, data in memory (in HEX) are all shown in the table. The required information is:

- The generated control signals (**DA, AA, BA, WR, MB, MD, MW, FS**) on the diagram to perform the instruction.
- The **contents of memory and registers** after executing following 6 instructions.

$$R0 \leftarrow M[R1]$$

$$R0 \leftarrow R0 + 1$$

$$R1 \leftarrow M[R3]$$

$$R1 \leftarrow R0 + R1$$

$$M[R2] \leftarrow R1$$

$$M[R3] \leftarrow R0$$

Address memory

09	20
0A	A3
0B	21

2E	34
2F	A4
30	71

Microoperations	DA	AA	BA	WR	MB	MD	MW	FS
$R0 \leftarrow M[R1]$	000	001	XXX	1	0	1	0	XXXX
$R0 \leftarrow R0 + 1$	000	000	XXX	1	0	0	X	0001
$R1 \leftarrow M[R3]$	001	011	XXX	1	0	1	0	XXXX
$R1 \leftarrow R0 + R1$	001	000	001	1	0	0	X	0010
$M[R2] \leftarrow R1$	XXX	010	001	0	0	X	1	XXXX
$M[R3] \leftarrow R0$	XXX	011	000	0	0	X	1	XXXX

The contents of Registers and Memory are as shown:

R0 = 21

R1 = C5

R2 = 2E

R3 = 2F

address memory

09	20
0A	A3
0B	21

2E	C5
2F	21
30	71

Question 6 (6 Marks: 3+3)

(a)

TABLE 8-8
Instruction Specifications for the Simple Computer

Instruction	Opcode	Mne- monic	Format	Description	Status Bits
Move A	0000000	MOVA	RD, RA	$R[DR] \leftarrow R[SA]^*$	N, Z
Increment	0000001	INC	RD, RA	$R[DR] \leftarrow R[SA] + 1^*$	N, Z
Add	0000010	ADD	RD, RA, RB	$R[DR] \leftarrow R[SA] + R[SB]^*$	N, Z
Subtract	0000101	SUB	RD, RA, RB	$R[DR] \leftarrow R[SA] - R[SB]^*$	N, Z
Decrement	0000110	DEC	RD, RA	$R[DR] \leftarrow R[SA] - 1^*$	N, Z
AND	0001000	AND	RD, RA, RB	$R[DR] \leftarrow R[SA] \wedge R[SB]^*$	N, Z
OR	0001001	OR	RD, RA, RB	$R[DR] \leftarrow R[SA] \vee R[SB]^*$	N, Z
Exclusive OR	0001010	XOR	RD, RA, RB	$R[DR] \leftarrow R[SA] \oplus R[SB]^*$	N, Z
NOT	0001011	NOT	RD, RA	$R[DR] \leftarrow \neg R[SA]^*$	N, Z
Move B	0001100	MOVB	RD, RB	$R[DR] \leftarrow R[SB]^*$	
Shift Right	0001101	SHR	RD, RB	$R[DR] \leftarrow sr R[SB]^*$	
Shift Left	0001110	SHL	RD, RB	$R[DR] \leftarrow sl R[SB]^*$	

Load Immediate	1001100	LDI	RD, OP	$R[DR] \leftarrow zf\ OP^*$	
Add Immediate	1000010	ADI	RD, RA, OP	$R[DR] \leftarrow R[SA] + zf\ OP^*$	N, Z
Load	0010000	LD	RD, RA	$R[DR] \leftarrow M[SA]^*$	
Store	0100000	ST	RA, RB	$M[SA] \leftarrow R[SB]^*$	
Branch on Zero	1100000	BRZ	RA, AD	if $(R[SA] = 0)$ $PC \leftarrow PC + se\ AD$, N, Z if $(R[SA] \neq 0)$ $PC \leftarrow PC + 1$	
Branch on Negative	1100001	BRN	RA, AD	if $(R[SA] < 0)$ $PC \leftarrow PC + se\ AD$, N, Z if $(R[SA] \geq 0)$ $PC \leftarrow PC + 1$	
Jump	1110000	JMP	RA	$PC \leftarrow R[SA]^*$	

* For all of these instructions, $PC \leftarrow PC + 1$ is also executed to prepare for the next cycle.

Consider Table 8-8 containing instruction specification for a simple computer. Translate the following instructions into 16-bit binary machine codes. (**NB:** use 0 for don't care)

Instruction	Binary machine code			
	Opcode	RD/AD(left)	RA	RB/OP/AD(Right)
LDI R5, 5	1001100	101	000	101
SUB R3, R5, R1	0000101	011	101	001
ST (R6), R1	0100000	000	110	001
SHR R0, R2	0001101	000	000	010
BRZ R5 AD (AD = 101 011)	1100000	101	101	011
JMP R6	1110000	000	110	000

- (b) Assume that an array A with 4 elements is located at the address 200 in data memory containing values shown in the figure. Write an assembly language program to calculate the summation of all elements in the array and store the **average** in variable S is located at the address 220. (**NB:** use register R0 as an address register only).

address	memory
...	...
200	2
201	83
202	-21
203	98
...	...
220	...

(c)

LDI R0, 200	INC R0, R0
LD R1, (R0)	LD R2, (R0)
	ADD R1, R1, R2
INC R0, R0	
LD R2, (R0)	SHR R1, R1
ADD R1, R1, R2	SHR R1, R1
INC R0, R0	LDI R0, 220
LD R2, (R0)	ST (R0), R1
ADD R1, R1, R2	

THE END