

QUESTION 9

How many 512 x 16 RAM chips are needed to provide a memory capacity of 2 kilo Bytes?

☐ 4

☐ 16

☐ 8

☒ 2

☐ None



$$(2 \cdot 2^{10} \text{ B}) \left(\frac{8 \text{ bit}}{1 \text{ B}} \right) = 16384 \text{ bit}$$

$$(512)(16)y = 16384 \Rightarrow y = 2$$

Question 5**1 points**

Save Answer

Suppose 8-bit registers **R1** = 1010 0111, **R2** = 0001 0101, where 2's complement signed number system is used. What will be the content of **R3** after the micro-operations: $R3 \leftarrow R1 \wedge R2$?

R3 = [A]

00000101

$$\begin{array}{r} 10100111 \\ \text{AND } 00010101 \\ \hline R_3 = 00000101 \end{array}$$



Moving to another question will save this response.

« « Question 5 of 10 » »

Close Window

Remaining Time: 34 minutes, 58 seconds.

▼ Question Completion Status:

QUESTION 1

1 points

A digital computer has a common bus system for 16 registers of 32 bit each. The bus is constructed with multiplexers. How many selection inputs are there in each multiplexer?

☐ 5

☐ 2

☐ 3

☒ 4

☐ None

32 muxs

16 to 1 mux

$$2^4 = 16$$

QUESTION 2

1 points

Question Completion Status:

QUESTION 2

1 points

The content of a 8-bit register is initially 11101101. The register is shifted 2 times to the right with the serial input being 0 and 1 respectively. What is the content of the register after each shift operation?

After first shift 01110110

✓

After second shift 10111011

X

10111011

10111011

QUESTION 3

1 points

Suppose 8-bit registers $R_1 = 1010\ 0111$, $R_2 = 0001\ 0101$, where 2's complement signed number system is used. What will be the content of R_3 after the micro-operations: $R_3 \leftarrow R_1 - R_2$?

$R_3 = [A]$

10010010

$$\begin{array}{r} R_1 = 10100111 \\ -R_2 = 11101011 \\ \hline R_3 = 10010010 \end{array}$$

Question 10

1 points

Save Answer

What are the roles of the direct inputs (PS and PR) in a flip-flop?

Rich text editor toolbar: Bold, Italic, Underline, Arial, 3 (12pt), Text color, Bulleted list, Numbered list, Link, Unlink, Insert link, Insert image, Full screen, Help, Close.

They are used to initialize the flip-flop

Path: p » span Words:0

⚠ Click **Submit** to complete this assessment.

⏪ ⏩ Question 10 of 10

Question 3

1 points

Save Answer

Suppose 8-bit registers $R_1 = 0001\ 0101$, $R_2 = 1010\ 0111$, where 2's complement signed number system is used. What will be the content of R_3 after the micro-operations: $R_3 \leftarrow R_1 - R_2$?

$R_3 = [A]$

01101110

$$\begin{array}{r} R_1 = 00010101 \\ - R_2 = 10101001 \\ \hline R_3 = 01101110 \end{array} +$$

⏪ ⚠ Moving to another question will save this response.

⏪ ⏩ Question 3 of 10 ⏪ ⏩

Close Window

Question 9

1 points

Save Answer

How many 256 x 16 RAM chips are needed to provide a memory capacity of 4 kilo Bytes?

- ☐ None
- ☐ 2
- ☐ 16
- ☐ 4
- ☒ 8

$$\rightarrow (4 \cdot 2^{10} \text{ B}) \left(\frac{8 \text{ bit}}{1 \text{ B}} \right) = 32768$$

$$(256 \cdot 16) y = 32768 \Rightarrow y = 8$$

⚠ Moving to another question will save this response.

⏪ ⏩ Question 9 of 10 ⏪ ⏩

Close Window

Question 6

1 points

Save Answer

The content of a 8-bit register is initially 11101101. The register is shifted 2 times to the left with the serial input being 1 and 0 respectively. What is the content of the register after each shift operation?:

After first shift

~~11101101~~

After second shift

~~11011011~~

⏪ ⚠ Moving to another question will save this response.

⏪ ⏩ Question 6 of 10 ⏪ ⏩




Close Window

⚠ Moving to another question will save this response.

Question 5

What are the roles of the direct inputs (PS and PR) in a flip-flop?

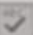For the toolbar, press ALT+F10 (PC) or ALT+FN+F10 (Mac).

B **I** **I** Arial ▼ 3 (12pt) ▼ **T** - ☰ - ☷ -  -  



QUESTION 10

We want to design a Hex to binary encoder.

How many inputs are there?

16

How many outputs are there?

4

Click Save and Submit to save and submit. Click Save All Answers to save all answers.

Type here to search



Close Window

⚠ Moving to another question will save this response.

Question 4 of 10

Question 4

1 points Save Answer

What are the roles of the direct inputs (PS and PR) in a flip-flop?

3 (12pt)



Path: 0

Type here to search



QUESTION 7

5 selections

We want to implement a Boolean function $F(A, B, C, D, E)$ with a multiplexer.

What will be the size of the multiplexer? $2^5 \text{ to } 1 \Rightarrow 32 \text{ to } 1$

How many selection inputs are there? 5

QUESTION 8

How many 512 x 16 RAM chips are needed to provide a memory capacity of 2 kilo Bytes?

☐ None

☐ 4

☐ 8

☒ 2 ✓

☐ 16

↓
 $(2 \cdot 2^{10} \text{ B})(8 \text{ bit}) = 16384$

$$(512 \cdot 16) y = 16384 \Rightarrow y = 2$$

QUESTION 9

A digital computer has a common bus system for 16 registers of 32 bit each. The bus is constructed with m there in each multiplexer?

Click Save and Submit to save and submit. Click Save All Answers to save all answers.

32 muxs

16 to 1 mux

$$2^4 = 16$$

4 selections

→ ⚠ Moving to another question will save this response.

Question 8

Determine the output frequency for a frequency division circuit that contains 2 flip-flops with an input clock frequency of 20.48 MHz.

- ☐ I. 5.12 kHz
- ☐ II. 10.24 kHz
- ☐ III. None
- ☐ IV. 10.12 MHz
- ☒ V. 5.12 MHz ✓

$$\frac{20.48}{2^2} = 5.12$$



Type here to search



Less than five minutes remain.

Close Window

⚠ Moving to another question will save this response.

Question 5 of 10

Question 5

1 points Save Answer

A digital computer has a common bus system for 32 registers of 16 bit each. The bus is constructed with multiplexers. How many selection inputs are there in each multiplexer?

- ☐ None
- ☐ 4
- ☒ 5
- ☐ 3
- ☐ 2

16 muxs
32 to 1 mux
 $2^5 = 32$
5 selections

Question 5 of 10

⚠ Moving to another question will save this response.

here to search



3:44 PM
4/28/2020

Question 1

اللي عنده علم يفيدنا بحل ذا السؤال

For 8 X 1 multiplexer, Nor of selection input is-----

☐ 2

☐ 4


☐ 1

☐ 3



$$2^3 = 8$$

3 selections

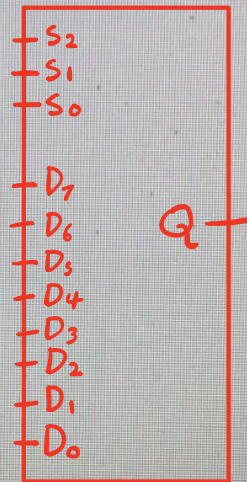


Moving to the next question prevents changes to this answer.



Moving to the next question prevents changes to this answer.

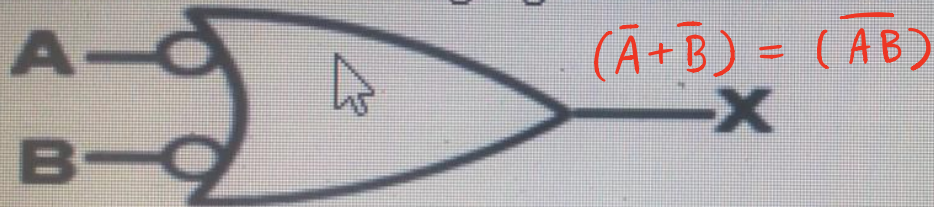Question 9

Which of the following logic functions is illustrated by following figure



☐ XOR X

☐ NOR X

☐ AND X

NAND ✓

Question 3

1 points

Save Answer

Suppose 8-bit registers $R_1 = 0001\ 0101$, $R_2 = 1010\ 0111$, where 2's complement signed number system is used. What will be the content of R_3 after the micro-operations: $R_3 \leftarrow R_1 - R_2$?

$R_3 = [A]$

01101110

$$\begin{array}{r} R_1 = 00010101 \\ -R_2 = 01011001 \quad + \\ \hline R_3 = 01101110 \end{array}$$

⏪ ⚠ Moving to another question will save this response.

⏪ ⏩ Question 3 of 10 ⏪ ⏩

Close Window

QUESTION 2

1 points

Save Answer

Suppose 8-bit registers $R1 = 0001\ 0101$, $R2 = 1010\ 0111$, where 2's complement signed number system is used. What will be the content of $R3$ after the micro-operations: $R3 \leftarrow R1 \oplus R2$?

$R3 = [A]$

10110010

$$\begin{array}{r} 00010101 \\ \text{XOR } 10100111 \\ \hline R_3 = 10110010 \end{array}$$

Question 1

s selections

1 points

✓ Saved

We want to implement a Boolean function $F(A, B, C, D, E)$ with a demultiplexer.

What will be the size of the demultiplexer?

5

How many selection inputs are there?

32

$$2^5 = 32$$

⏪ ⚠ Moving to another question will save this response.

Question 1 of 10 > >>

Close Window

Question 5

1 points

Save Answer

Suppose 8-bit registers $R1 = 1010\ 0111$, $R2 = 0001\ 0101$, where 2's complement signed number system is used. What will be the content of $R3$ after the micro-operations: $R3 \leftarrow R1 \wedge R2$?

$R3 = [A]$

0000101

AND

	1	0	1	0	0	1	1
	0	0	0	1	0	1	0
<hr/>							
	0	0	0	0	1	0	1



Moving to another question will save this response.

« « Question 5 of 10 » »

Close Window

⏪ ⚠ Moving to another question will save this response.

Question 1

How many flip-flops are required to construct an asynchronous MOD-200 counter?

☐ 10

☐ None

☐ 4

☒ 8

☐ 6

$$2^8 = 256$$

Remaining Time: 31 minutes, 36 seconds.

Question Completion Status:

⚠ Moving to another question will save this response.

Question 1

What are the roles of the direct inputs (PS and PR) in a flip-flop?

T T T Arial 3 (12pt) T : : : ✓



Path: p

⚠ Moving to another question will save this response.

Question 2

1 points

Save Answer

A digital computer has a common bus system for 32 registers of 16 bit each. The bus is constructed with multiplexers. How many selection inputs are there in each multiplexer?


- ☐ 3
- ☒ 5 ✓
- ☐ None
- ☐ 4
- ☐ 2

16 muxs
32 to 1 mux
 $2^5 = 32$
5 selections

→ ⚠ Moving to another question will save this response.

⏪ ⏩ Question 2 of 10 ⏪ ⏩

Question 4

1 points  Saved

How many flip-flops are required to construct an asynchronous MOD-200 counter?

- ☒ 6
- ☐ 8
- ☐ 10
- ☐ 4
- ☐ None

⏪ ⚠ Moving to another question will save this response.

⏪ ⏩ Question 4 of 10 ⏪ ⏩

Close Window

QUESTION 10

5 selections

We want to implement a Boolean function $F(A, B, C, D, E)$ with a multiplexer.

What will be the size of the multiplexer?

32 to 1

How many selection inputs are there?

5

Question 7

1 points

Save Answer

We want to design a decimal to BCD encoder.

How many inputs are there?

How many outputs are there?

⏏ ⚠ Moving to another question will save this response.

⏪ ⏩ Question 7 of 10 ⏪ ⏩

Close Window