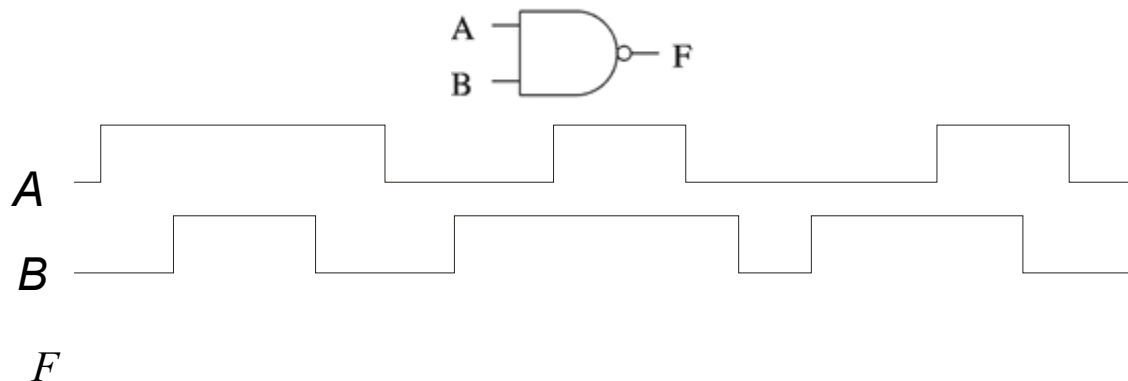




Tutorial-2: Logic Gates and Functions

Q1: Given the wave-forms for input A and B for the following NAND gate. Draw the output wave-form for F.



Q 2: Given the function $f(A, B, C, D) = \Sigma(2, 3, 5, 6, 7, 9, 11, 13)$

- i. Write the output expression in SOP form
- ii. Implement it with basic logic gates


Q3: An n -bit even parity generator will produce an extra bit based on n input bits – it will produce 1 if number of 1's in n input bits is odd, 0 otherwise (e.g. for 4-bit input 0111 the extra bit will be 1, and for 1001 it will be 0).

- i. Give the truth table for four-bit parity generator using even parity bit
- ii. Write the output expression in SOP form
- iii. Write the output expression in POS form.


Q4: A majority function is generated in a combinational circuit when the output is equal to 1 if the input variables have more 1's than 0's, the output is 0 otherwise.

- i. Give truth table four-input majority function
- ii. Write the output expression in SOP form
- iii. Draw the logic circuit.

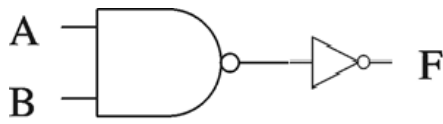Q5: Using truth table, show that the following two circuits are logically equivalent.



(a)

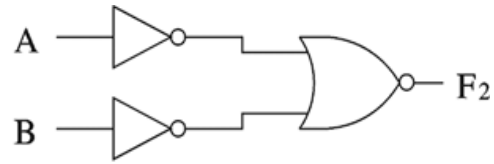

(b)

Home Works

Text book problems: 2-11, 2-13, 3-1, 3-3, 3-8

Additional Problems

1: Which of the following Boolean equations describes the circuit of Fig. 2.5.2?

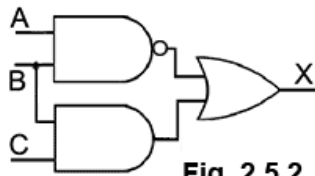


Fig. 2.5.2

- a) $X = (A \cdot B)' + (B \cdot C)$ b) $X = (A \cdot B) \cdot (B + C)$
 c) $X = (A \cdot B) + (B \cdot C)$ d) $X = (A \cdot B) + C$

2: Which of the following logic functions is illustrated by Fig. 2.5.3?



Fig.2.5.3

- a) XOR b) NOR c) AND d) NAND

3. Design four-bit parity generator using odd parity bit.

- Give the truth table
- Write the output expression in SOP form
- Draw the logic circuit.