



### **Tutorial 3: K-map**

**Q1:** Given the function  $f(A, B, C) = \Sigma(0, 1, 3, 5, 7)$

- i. Simplify the function with K-map
- ii. Implement it with basic logic gates.

**Q2:** Given the function  $f(A, B, C, D) = \Sigma(2, 3, 5, 6, 7, 9, 11, 13)$

- i. Simplify the function with K-map
- ii. Implement it with basic logic gates.

**Q3:** Simplify the following function with K-map

$$f(A, B, C, D) = \Sigma_m(2, 5, 6, 9, 10, 12, 13, 14) + \Sigma_d(3, 7, 11, 15)$$

- i. Implement it with basic logic gates.
- ii. Implement it with only NAND gates.
- iii. Implement it with only NOR gates.

### **Home Works**

**Text book problems: 2-14 to 2-17, 2-19, 2-20, 2-25**