

Question 1. (8 Marks)

Q#1.a Marks 4

1) Write octal number corresponds to the hexadecimal number EF.C

(357.6)₈

2) Write Binary number that corresponds to the decimal number 45.125

(101101.001)₂

3) Write BCD code corresponds to the binary number 1101.1

(0001 0011 . 0101)_{BCD}

4) Write The decimal number corresponds to the octal number 21.4

(17.5)₁₀

Q#1.b

Write smallest and largest Positive and negative number represented in 6 bits representation in 2's complement. Mark 1

Ans: Largest: +31

Smallest: -32

Q#1.C


Complete following Table

Marks 3

A	A in Sign Magnitude (8 bits)	A in 1's Comp. (8 bits)	A in 2's comp. (8 bits)
10	00001010	00001010	00001010
-1	10000001	11111110	11111111
-7	10000111	11111000	11111001

Question 2 (6 Marks: 2+2+2)

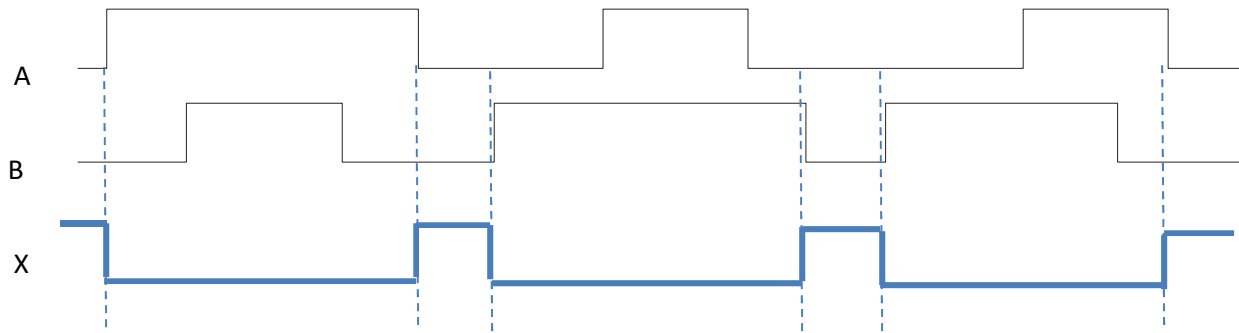(a) Suppose A and B are input waveform for a NOR Gate, show the output waveform X



(b) Suppose a combinational circuit accepts a 3-bit binary number and generate a 4-bit binary output equal to double of the input number (e.g. if input is 011 the output is 0110).

- Write the truth table for the function
- Represent the functions in SOP form (without simplification).

Answer of Question 2 (b)

A	B	C	w	x	y	z
0	0	0	0	0	0	0
0	0	1	0	0	1	0
0	1	0	0	1	0	0
0	1	1	0	1	1	0
1	0	0	1	0	0	0
1	0	1	1	0	1	0
1	1	0	1	1	0	0
1	1	1	1	1	1	0

$$w = \sum m(4, 5, 6, 7)$$

$$x = \sum m(2, 3, 6, 7)$$

$$y = \sum m(1, 3, 5, 7)$$

$$z = 0$$

Question 3 (5 Marks: 2+1+2)

(a) Find the Simplified function of Boolean function F together with the don't-care conditions d in sum-of-products form

$$F(w, x, y, z) = \sum (0, 1, 2, 3, 7, 8, 10)$$


$$d(w, x, y, z) = \sum (5, 6, 11, 15)$$

(b) Find the Simplified function of the following Boolean function in sum-of-products form by means of a four-variable k-map.

$$F(w, x, y, z) = \sum m(0, 1, 8, 9, 10, 12, 13)$$


(c) Draw the logic diagram of simplified function of (b) with NAND gates only.

Answer of Question 3 (a)

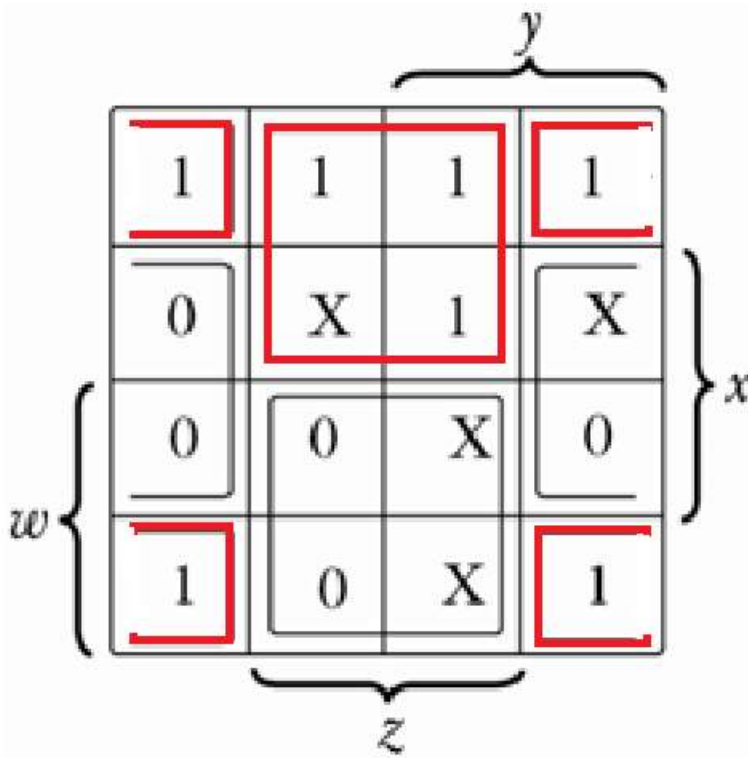


$$F = x'z' + w'z$$

Answer of Question 3 (b)

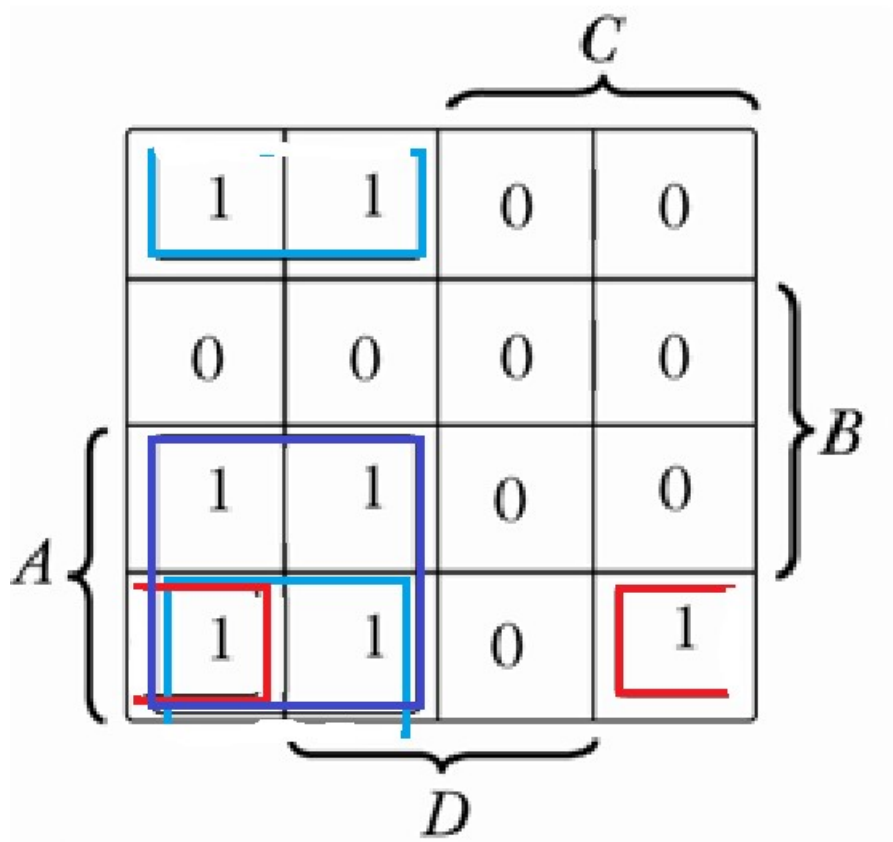


$$F = AC' + B'C' + AB'D'$$

Answer of Question 3 (c)

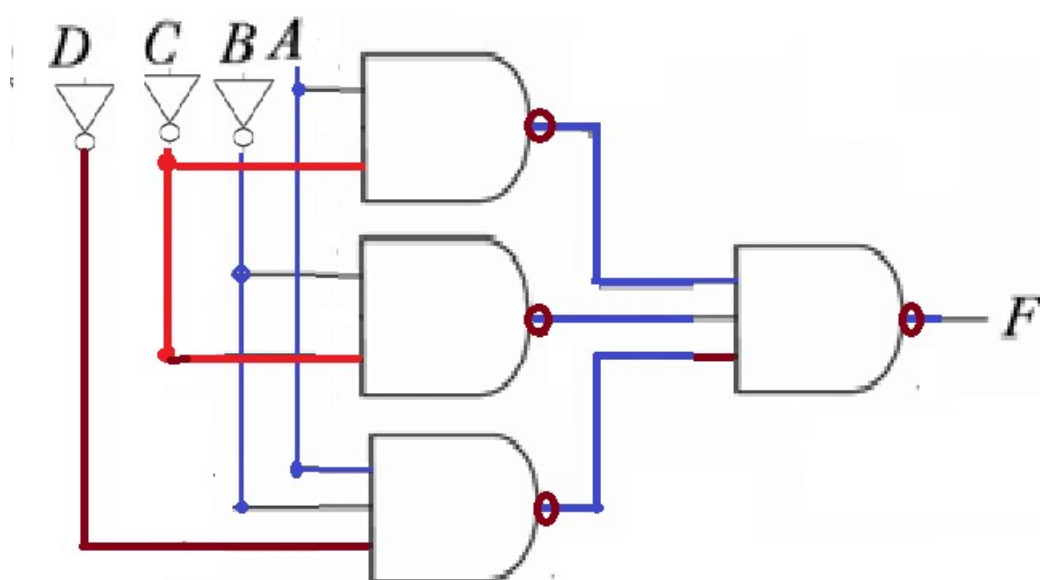

Question 4 (6 Marks: 2+2+2)

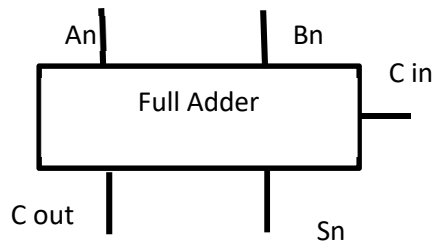(a) Consider the following bloc diagram of a full-adder




Give the truth table of the circuit and drive the output expressions of S_n and C_{out} .

A_n	B_n	C_{in}	S_n	C_{out}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1


$$C_{out} = (A_n \oplus B_n)C_{in} + A_nB_n$$

$$S = A_n \oplus B_n \oplus C_{in}$$

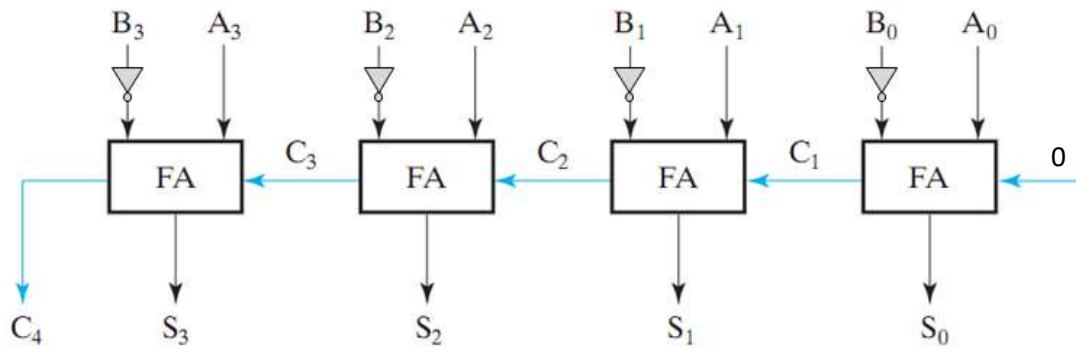(b) Using this circuit show how can we built a circuit capable of performing the subtraction, using 2's complement method, between two words A and B of 4 bits each one.



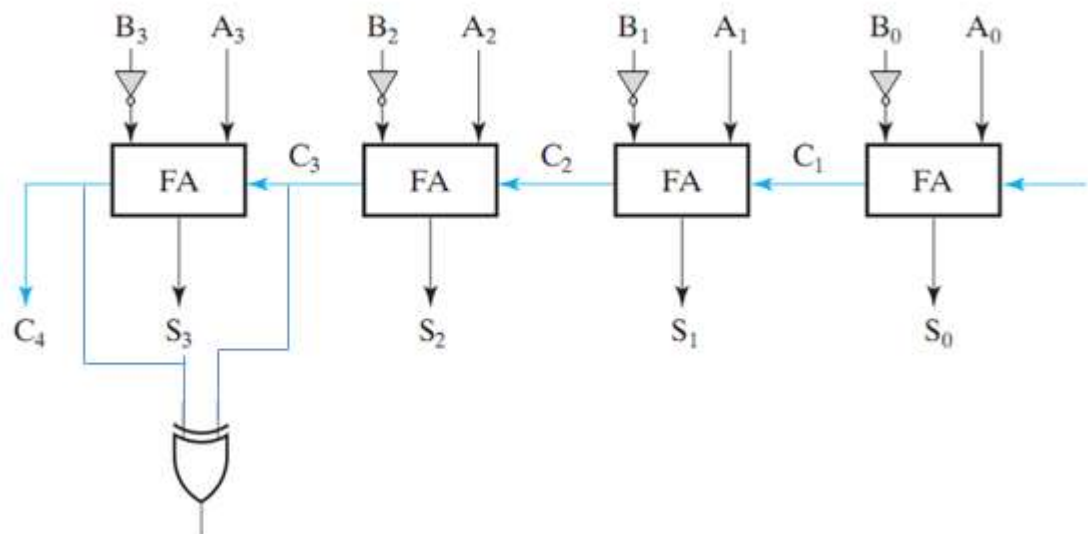(c) Give a solution to detect sign overflow for the circuit that is proposed in (b)



Sign overflow bit

THE END