



Labwork – 8


Name: Muaid Almutairi

ID: 442101942

1. Introduction

Today I learn how to draw use clock, register, splitter and more tools to design the bus.

2. Experiments

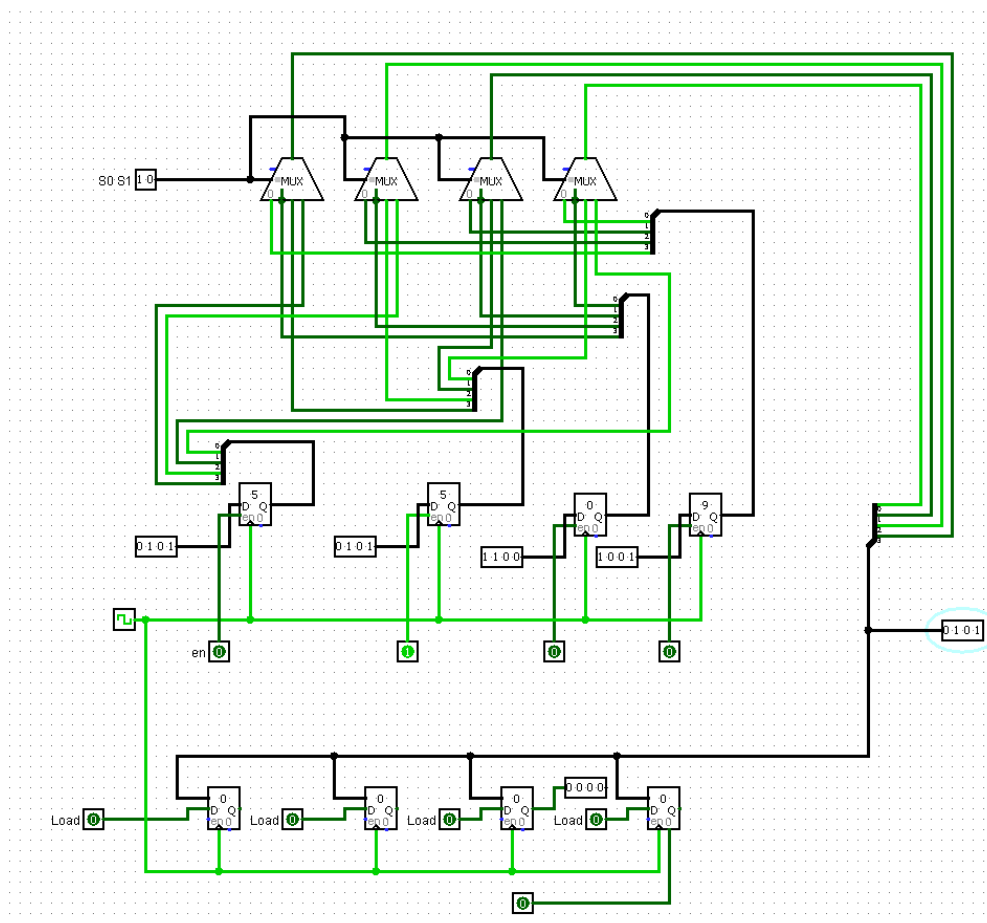

3. Results

I transferred data from register D to register A and B.

4. Discussion

We can execute a Register circuit and how the bus goes on. We use four multiplexer and four register which are connected in a specific links contains splitters. Then connected with a clock.