



King Saud University
College of Computer and Information Sciences
Department of Computer Science

CSC 220: Computer Organization

Tutorial 7: Flip Flop



Q1:

- Give the transition table and Represent the synchronous SR Flip Flop with NAND gates.
- Explain the role of the control signal in the function of SR Flip Flop
- Explain how to obtain D Flip Flop from the SR structure.


Q2:

- Give the transition table of JK Flip Flop.
- Show how to implement a JK flip-flop using NAND gates
- Explain how to obtain T Flip Flop from the JK structure.

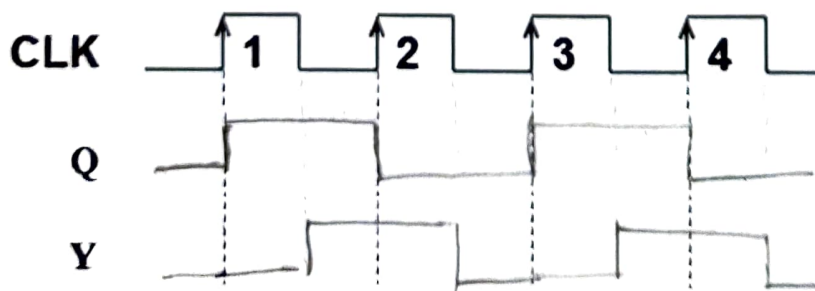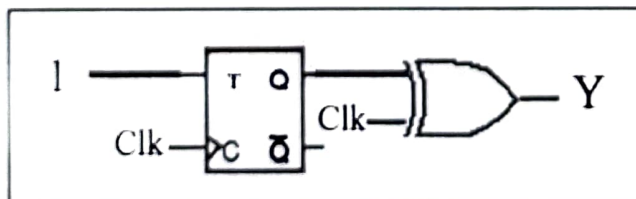Q3: For the given diagram below- what will be the output waveform at Q and Y (assuming that initially Q = 0)?




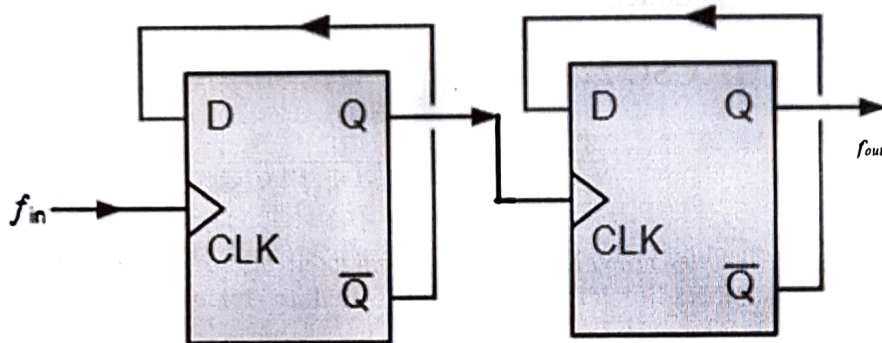Q4: Determine the output frequency (f_{out}) for a frequency division circuit that contains 2 flip-flops with an input clock frequency of 20.48 MHz.



$$f_{out} = 20'48 / 2^2 = 20'48 / 4 = 5'12 \text{ MHz}$$

Q5: Consider the following JK Flip Flop.

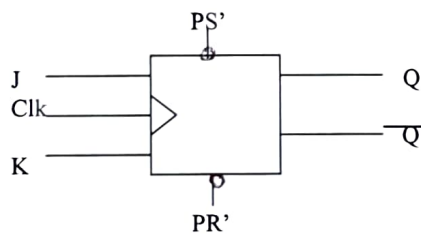

- Explain the role of the direct inputs (PS and PR) with characteristic table.
- Represent the outputs of the JK Flip flop (s) for the following input signal waves .

