



CSC 220: Computer Organization

Unit 2 Digital Circuit Design

Prepared by:
Md Saiful Islam, PhD

Department of Computer Science
College of Computer and Information Sciences

Overview

- Digital Circuit Design
 - Logic Gates
 - Logic Functions
 - Standard Forms (SOP/POS)
- Universal Gates (NAND/NOR)
- XOR and XNOR Gates
- Logical Equivalence
- Logic Chips

Chapter-2

M. Morris Mano, Charles R. Kime and Tom Martin, **Logic and Computer Design Fundamentals**, Global (5th) Edition, Pearson Education Limited, 2016. ISBN: 9781292096124



Digital Circuit

- ▶ **Digital Circuit** (hardware) manipulate binary information

- ▶ **Input-output:** one or more binary values



- ▶ Hardware consists of a few simple building blocks called *logic gates*
- ▶ **Logic gate:** a electronic device the operates on one or more input signals and produce an output.
 - ▶ **Basic Logic gates:** AND, OR, NOT, ...
 - ▶ **Additional gates:** NAND, NOR, XOR, XNOR...
- ▶ Logic gates are built using transistors
 - ▶ NOT gate can be implemented by a single transistor
 - ▶ AND-OR gate requires 3 transistors
- ▶ Transistors are the fundamental devices
 - ▶ Pentium consists of 3 million transistors
 - ▶ Compaq Alpha consists of 9 million transistors
 - ▶ Now we can build chips with more than 100 million transistors



Logic Gates

▶ Basic gates


- ▶ **AND**
- ▶ **OR**
- ▶ **NOT**

▶ Functionality can be expressed by a truth table

- ▶ A truth table lists output for each possible input combination


▶ Precedence

 - ▶ NOT > AND > OR
- ▶ $F = A \bar{B} + \bar{A} B$
 $= (A (\bar{B})) + ((\bar{A}) B)$




AND gate

A	B	F
0	0	0
0	1	0
1	0	0
1	1	1

 

OR gate

A	B	F
0	0	0
0	1	1
1	0	1
1	1	1

 

NOT gate


A	F
0	1
1	0

Logic symbol


Truth table

Logic Gates ...

 
- ▶ Additional useful gates
 - ▶ NAND
 - ▶ NOR
 - ▶ XOR
 - ▶ XNOR
- ▶ NAND = AND + NOT
- ▶ NOR = OR + NOT
- ▶ NAND and NOR gates require only 2 transistors
 - ▶ AND and OR need 3 transistors!
- ▶ XOR implements exclusive-OR function
- ▶ XNOR is complement of XOR



NAND gate

 

NOR gate

 

XOR gate

Logic symbol

A	B	F
0	0	1
0	1	1
1	0	1
1	1	0

A	B	F
0	0	1
0	1	0
1	0	0
1	1	0

A	B	F
0	0	0
0	1	1
1	0	1
1	1	0

Truth table

Logic Functions

- ▶ A logic circuit implements a Boolean function.

- ▶ A Boolean function consists of

- ▶ Binary variables
- ▶ Constants 0, 1
- ▶ Logic operators: AND (.), OR (+), NOT(-), ...



- ▶ A function with N input variables

- ▶ With N logical variables, we can define

2^N combination of inputs

- ▶ A **single-output function** relates the output (0/1) to inputs
- ▶ Multiple-output Boolean function
 - ▶ More than one outputs
 - ▶ Each output (0/1) is related to same inputs



Logic Functions ...

▶ Designing a Logic Circuit (4 steps)

- ▶ Step 1: Represent a logic function using a truth table
- ▶ Step 2: Obtain a logical expression from truth table
- ▶ Step 3: Simplify the function
- ▶ Step 4: Transfer the function to logic diagram of the circuit

▶ Example:

- ▶ Majority function
 - ▶ Output is one whenever majority of inputs is 1
 - ▶ We use 3-input majority function



Logic Functions ...

► Truth Table:

3-input majority function

A	B	C	F
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1


► Logical expression form

$$F = A'BC + AB'C + ABC' + ABC$$

► Simplification

$$F = AB + BC + AC$$

► Logic Diagram

 

Standard Forms

Standard Forms Boolean Expressions

- Sum-of-Products (SOP)
 - Derived from the Truth table for a function by considering those rows for which $F = 1$.
 - The logical sum (OR) of product (AND) terms.
 - Realized using an AND-OR circuit.
- Product-of-Sums (POS)
 - Derived from the Truth table for a function by considering those rows for which $F = 0$.
 - The logical product (AND) of sum (OR) terms.
 - Realized using an OR-AND circuit.




Sum of products expressions

- There are many equivalent ways to write a function, but some forms turn out to be more useful than others.
- A **sum of products** or **SOP** expression consists of:
 - One or more terms *summed* (OR'ed) together.
 - Each of those terms is a *product of literals*.

$$f(x, y, z) = y' + x'yz' + xz$$

 - Sum of products expressions can be implemented with **two-level circuits**.



Minterms

- A **minterm** is a special product of literals, in which each input variable appears exactly once.
- A function with n input variables has 2^n possible minterms.
- For instance, a three-variable function $f(x,y,z)$ has 8 possible minterms:

$$\begin{array}{cccc} x'y'z' & x'y'z & x'y z' & x'y z \\ x y'z' & x y'z & x y z' & x y z \end{array}$$

- Each minterm is true for exactly one combination of inputs.

Row number	x_1	x_2	x_3	Minterm	Maxterm
0	0	0	0	$m_0 = \bar{x}_1 \bar{x}_2 \bar{x}_3$	$M_0 = x_1 + x_2 + x_3$
1	0	0	1	$m_1 = \bar{x}_1 \bar{x}_2 x_3$	$M_1 = x_1 + x_2 + \bar{x}_3$
2	0	1	0	$m_2 = \bar{x}_1 x_2 \bar{x}_3$	$M_2 = x_1 + \bar{x}_2 + x_3$
3	0	1	1	$m_3 = \bar{x}_1 x_2 x_3$	$M_3 = x_1 + \bar{x}_2 + \bar{x}_3$
4	1	0	0	$m_4 = x_1 \bar{x}_2 \bar{x}_3$	$M_4 = \bar{x}_1 + x_2 + x_3$
5	1	0	1	$m_5 = x_1 \bar{x}_2 x_3$	$M_5 = \bar{x}_1 + x_2 + \bar{x}_3$
6	1	1	0	$m_6 = x_1 x_2 \bar{x}_3$	$M_6 = \bar{x}_1 + \bar{x}_2 + x_3$
7	1	1	1	$m_7 = x_1 x_2 x_3$	$M_7 = \bar{x}_1 + \bar{x}_2 + \bar{x}_3$

Sum of minterms expressions

- A **sum of minterms** is a special kind of sum of products.
- Every function can be written as a *unique* sum of minterms expression.
- A truth table for a function can be rewritten as a sum of minterms just by finding the table rows where the function output is 1.

x	y	z	$C(x,y,z)$	$C'(x,y,z)$
0	0	0	0	1
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	0

$$\begin{aligned}C &= x'yz + xy'z + xyz' + xyz \\&= m_3 + m_5 + m_6 + m_7 \\&= \Sigma m(3,5,6,7)\end{aligned}$$

$$\begin{aligned}C' &= x'y'z' + x'y'z + x'yz' + xy'z' \\&= m_0 + m_1 + m_2 + m_4 \\&= \Sigma m(0,1,2,4)\end{aligned}$$

C' contains all the minterms *not* in C , and vice versa.

Sum-of-Products

- Any function F can be represented by a sum of minterms, where each minterm is ANDed with the corresponding value of the output for F .

- $F = \sum (m_i \cdot f_i)$

Denotes the logical
sum operation

- where m_i is a minterm
 - and f_i is the corresponding functional output

- Only the minterms for which $f_i = 1$ appear in the expression for function F .

- $F = \sum (m_i) = \sum m(i)$ ← shorthand notation

- Sum of minterms are a.k.a. Canonical Sum-of-Products
- Synthesis process
 - Determine the Canonical Sum-of-Products
 - Use Boolean Algebra (and K-maps) to find an optimal, functionally equivalent, expression.




Product of sums expressions

- As you might expect, we can work with the duals of these ideas too.
- A **product of sums** or **POS** consists of:
 - One or more terms *multiplied* (AND'ed) together.
 - Each of those terms is a *sum of literals*.

$$g(x, y, z) = y'(x' + y + z')(x + z)$$

 - Products of sums can also be implemented with **two-level circuits**.



Maxterms

- A **maxterm** is a *sum* of literals where each input variable appears once.
- A function with n input variables has 2^n possible maxterms.
- For instance, a function with three variables x , y and z has 8 possible maxterms:

$$\begin{array}{cccc} x + y + z & x + y + z' & x + y' + z & x + y' + z' \\ x' + y + z & x' + y + z' & x' + y' + z & x' + y' + z' \end{array}$$

- Each maxterm is *false* for exactly one combination of inputs.

Row number	x_1	x_2	x_3	Minterm	Maxterm
0	0	0	0	$m_0 = \bar{x}_1 \bar{x}_2 \bar{x}_3$	$M_0 = x_1 + x_2 + x_3$
1	0	0	1	$m_1 = \bar{x}_1 \bar{x}_2 x_3$	$M_1 = x_1 + x_2 + \bar{x}_3$
2	0	1	0	$m_2 = \bar{x}_1 x_2 \bar{x}_3$	$M_2 = x_1 + \bar{x}_2 + x_3$
3	0	1	1	$m_3 = \bar{x}_1 x_2 x_3$	$M_3 = x_1 + \bar{x}_2 + \bar{x}_3$
4	1	0	0	$m_4 = x_1 \bar{x}_2 \bar{x}_3$	$M_4 = \bar{x}_1 + x_2 + x_3$
5	1	0	1	$m_5 = x_1 \bar{x}_2 x_3$	$M_5 = \bar{x}_1 + x_2 + \bar{x}_3$
6	1	1	0	$m_6 = x_1 x_2 \bar{x}_3$	$M_6 = \bar{x}_1 + \bar{x}_2 + x_3$
7	1	1	1	$m_7 = x_1 x_2 x_3$	$M_7 = \bar{x}_1 + \bar{x}_2 + \bar{x}_3$

Product of maxterms expressions

- Every function can also be written as a unique **product of maxterms**.
- A truth table for a function can be rewritten as a product of maxterms just by finding the table rows where the function output is 0.

x	y	z	$C(x,y,z)$	$C'(x,y,z)$
0	0	0	0	1
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	0

$$\begin{aligned}
 C &= (x + y + z)(x + y + z') \\
 &\quad (x + y' + z)(x' + y + z) \\
 &= M_0 M_1 M_2 M_4 \\
 &= \prod M(0,1,2,4) \\
 &= \sum m(3,5,6,7)
 \end{aligned}$$

When the o/p is Zero

When the o/p is 1

$$\begin{aligned}
 C' &= (x + y' + z')(x' + y + z') \\
 &\quad (x' + y' + z)(x' + y' + z') \\
 &= M_3 M_5 M_6 M_7 \\
 &= \prod M(3,5,6,7)
 \end{aligned}$$

C' contains all the maxterms *not* in C , and vice versa.

Product-of-Sums

- Any function F can be represented by a product of Maxterms, where each Maxterm is ANDed with the *complement* of the corresponding value of the output for F .

- $F = \prod (M_i \cdot f'_i)$

- where M_i is a Maxterm

Denotes the logical
product operation

- and f'_i is the complement of the corresponding functional output


- Only the Maxterms for which $f_i = 0$ appear in the expression for function F .

- $F = \prod (M_i) = \prod M(i)$ ← shorthand notation


- The Canonical Product-of-Sums for function F is the Product-of-Sums expression in which each sum term is a Maxterm.
- Synthesis process
 - Determine the Canonical Product-of-Sums
 - Use Boolean Algebra (and K-maps) to find an optimal, functionally equivalent, expression.

Universal Gates

 
- ▶ NAND and NOR gates are called universal gates
- ▶ Proving NAND gate is universal



AND gate

 

NOT gate

 


OR gate




Universal Gates...


- ▶ Proving NOR gate is universal

 

OR gate

 

NOT gate

 


AND gate



XOR and XNOR Gates

The XOR Gate

 

The **XOR** gate produces a HIGH output only when the inputs are at opposite logic levels. The truth table is

Inputs		Output
A	B	X
0	0	0
0	1	1
1	0	1
1	1	0


The **XOR** operation is written as $X = \bar{A}B + A\bar{B}$.

Alternatively, it can be written with a circled plus sign between the variables as $X = A \oplus B$.


XOR and XNOR Gates ...

The XOR Gate


A
 B

 

A
 B

 

Example waveforms:

 


Notice that the XOR gate will produce a HIGH only when exactly one input is HIGH.


XOR and XNOR Gates ...

The **XNOR** Gate

A
 B

 

A
 B


 


The **XNOR** gate produces a HIGH output only when the inputs are at the same logic level. The truth table is


Inputs		Output
A	B	X
0	0	1
0	1	0
1	0	0
1	1	1

The **XNOR** operation can be shown as $X = AB + \bar{A}\bar{B}$.

The XNOR Gate

  

Example waveforms:

 


Notice that the XNOR gate will produce a HIGH when both inputs are the same. This makes it useful for comparison functions.


Logical Equivalence

- ▶ When two circuits implement same logic function

 
Example: All three circuits implement $F = A B$ function



(a)

 

(b)

 


(c)

Logical Equivalence ...

► Proving logical equivalence:

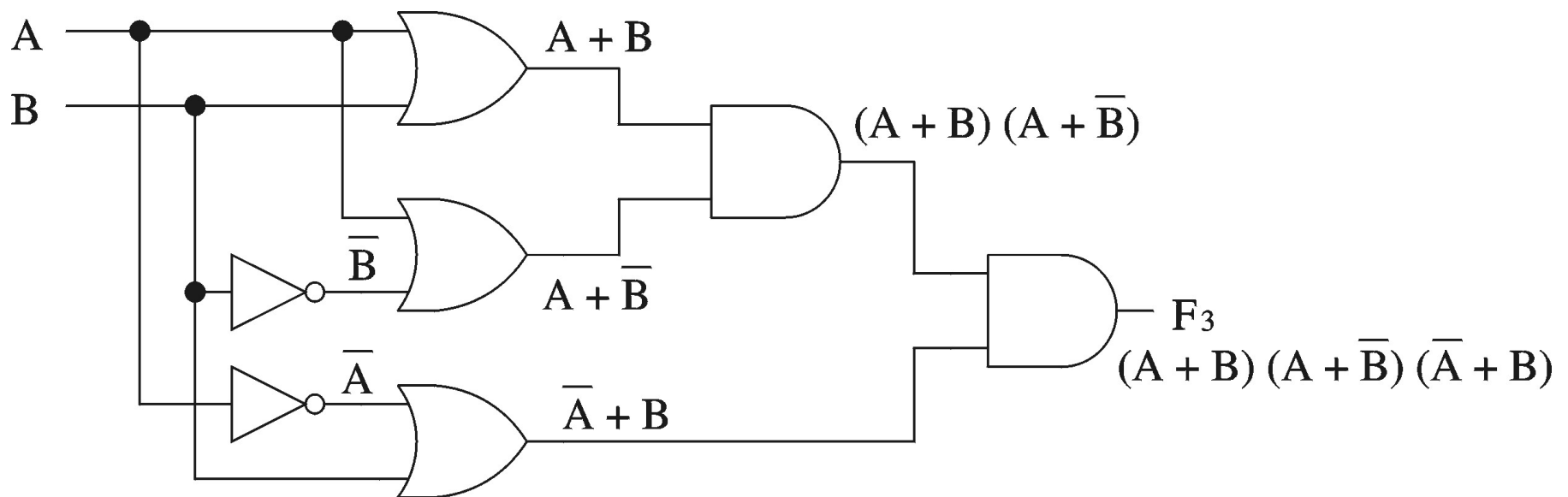- Derivation of logical expression from a circuit
 - Trace from the input to output
 - Write down intermediate logical expressions along the path
- Build the truth table relating inputs to the output for each circuit



Logical Equivalence ...




- ▶ Build the truth table for each circuit
- ▶ If each function give the same output, they are logically equivalent

A	B	$F1 = A B$	$F3 = (A + B) (\bar{A} + B) (A + \bar{B})$
0	0	0	0
0	1	0	0
1	0	0	0
1	1	1	1

- ▶ **Exercise:**

- ▶ Show that $X \oplus Y$ is logically equivalent to $X'Y + XY'$

Logic Chips

   

Logic Chips ...

▶ Integration levels

- ▶ SSI (small scale integration)
 - ▶ Introduced in late 1960s
 - ▶ 1-10 gates (previous examples)
- ▶ MSI (medium scale integration)
 - ▶ Introduced in late 1960s
 - ▶ 10-100 gates
- ▶ LSI (large scale integration)
 - ▶ Introduced in early 1970s
 - ▶ 100-10,000 gates
- ▶ VLSI (very large scale integration)
 - ▶ Introduced in late 1970s
 - ▶ More than 10,000 gates

