



King Saud University
College of Computer and Information Sciences
Department of Computer Science

CSC 220: Computer Organization


Labwork - 7

1. Introduction


In this lab we were asked to do two experiments, the first one is to design a logic diagram of a sequential circuit that has two D flip-flops and two inputs and one output, in the second experiment we were given a register designed by logic gates and D flip-flops and we were asked to design it.

2. Experiments

Ex1:

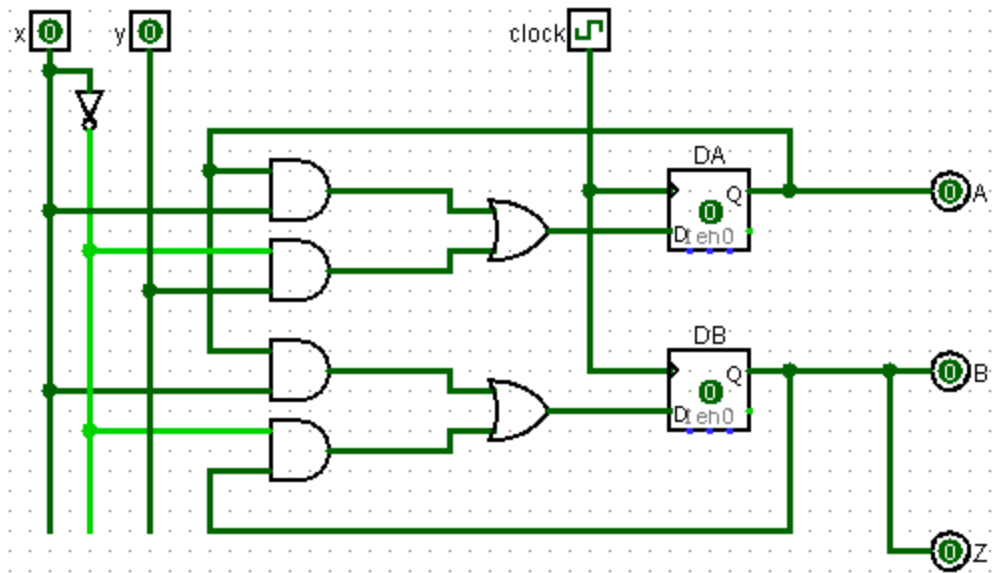

Ex2:

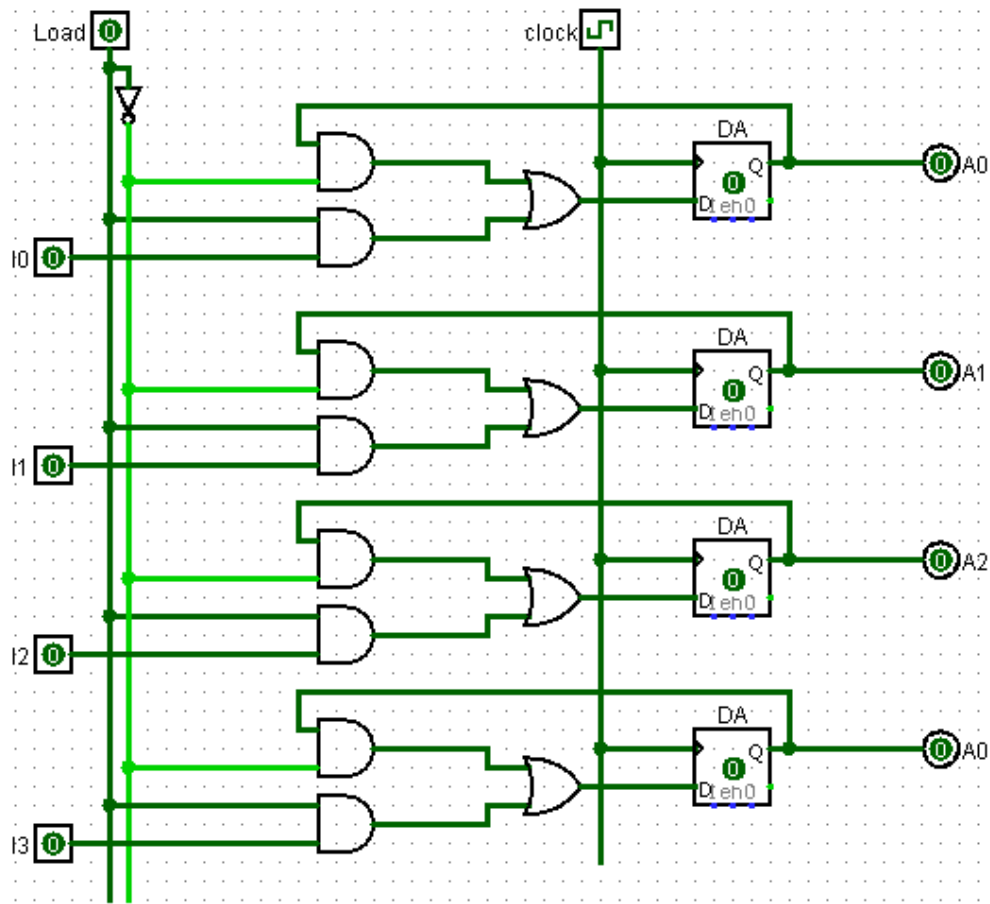

3. Results

Q1:

$$Da = x'y + xA$$

$$Db = x'B + xA$$

$$Z = B$$

Q2:

$$Da0 = Load'A0 + LoadI0$$

$$Da1 = Load'A1 + LoadI1$$

$$Da2 = Load'A2 + LoadI2$$

$$Da3 = Load'A3 + LoadI3$$

4. Discussion

In this week's lab we had two experiments, in the first one we designed a logic diagram for some equations given to us using basic logic gates and two D-flip flops and in the second experiment we designed using 4 D-flip flops.