


<p align="center">King Saud University College of Computer and Information Sciences Computer Science Department</p>			 <p>College of Computer & Information Sciences Computer Science Department</p>	
Course Code	CSC 220			
Course Title	Computer Organization			
Semester	S2 – 1440/1441 (Spring-2019-20)			
Exam	Midterm 1			
Date	05/03/2020	Duration	90 minutes	
Student Name				
Student ID				
Section No.				
Course Learning Outcomes		Relevant question	Full mark	Student mark
Knowledge	CLO 1, 2, 4	1	8	
Cognitive Skills	CLO 1, 2	2	6	
Cognitive Skills	CLO 1, 2, 4	3	6	
<p>Important Rules:</p> <ol style="list-style-type: none"> 1. Answer all questions 2. No calculator/electronic device is allowed during the exam <p>Feedback/Comments:</p>				

Question 1. (8 Marks: 5×1+3)

(a) Short Questions

- i. Convert 110110111_2 to Octal and Hexadecimal systems

Octal system	Hexadecimal system

- ii. Convert 46_{10} to Binary and to BCD

Binary system	BCD

- iii. Convert 10.25_{10} to Binary and to the Octal systems



Binary system	Octal system

- iv. Convert 14.2_8 to Binary and to Hexadecimal systems

Binary system	Hexadecimal system

- v. Show how to obtain AND and OR gate using only NOR gate.

Ans:

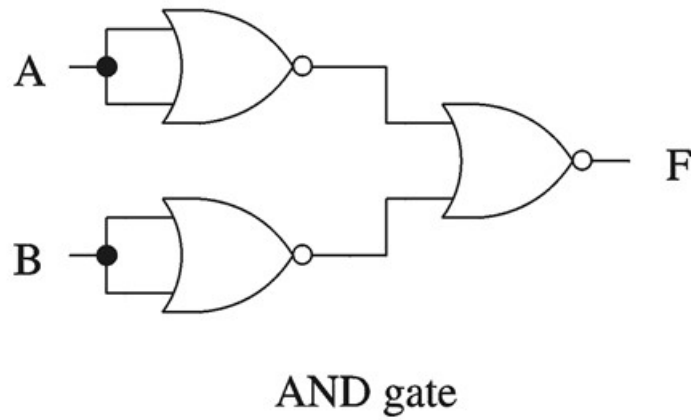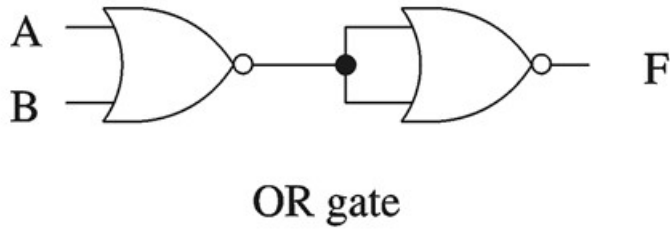

- (b) What will be the decimal value for the binary number 1010 1010 when it is represented in the following systems?
- Signed magnitude notation?
 - One's complements
 - Two's complements?

Ans:

- 32
- 85
- 86

Question 2 (6 Marks: 2+2+2)

- (a) The truth table for a logic circuit is given below. Obtain the logic expression of the circuit as sum of product (SOP) and implement the circuit with basic gates.

Inputs			Output
A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

- (b) Simplify the following logic expression using K-map and implement it using only NAND gates.

$$F(A, B, C, D) = \sum_m(0,4,7,8,15) + \sum_d(2,6,13,14)$$

(c) Represent the logic function $F(A, B, C) = \bar{A}\bar{B} + B + A\bar{B}C$ using NOR gates only.

Question 3 (6 Marks: 2+2+2)

(a) Given two decimal numbers $A = -25$ and $B = 17$, convert them into 2's complement representation using 8 bits and show how to obtain A-B.

Ans

A (2's comp. using 8 bits)	B (2's comp. using 8 bits)	A-B (2's comp. using 8 bits)
1110 0111	0001 0001	1101 0110

- (b) Design a full adder circuit (write the truth table, obtain the simplified functions, and implement them using logic gates).


Ans:

Truth table


X	Y	Z	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

$$S = X'Y'Z + X'YZ' + XY'Z' + XYZ = X \oplus Y \oplus Z$$
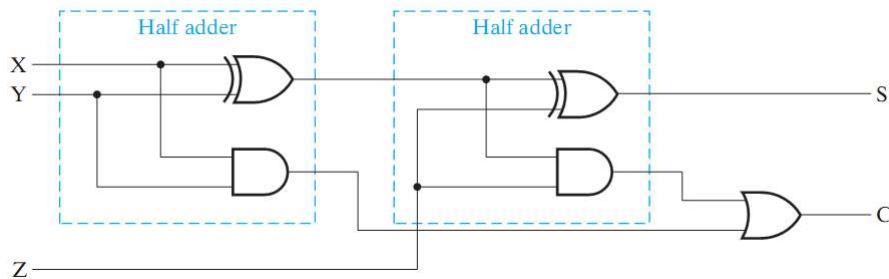
$$C = XY + XZ + YZ = XY + Z(X \oplus Y)$$



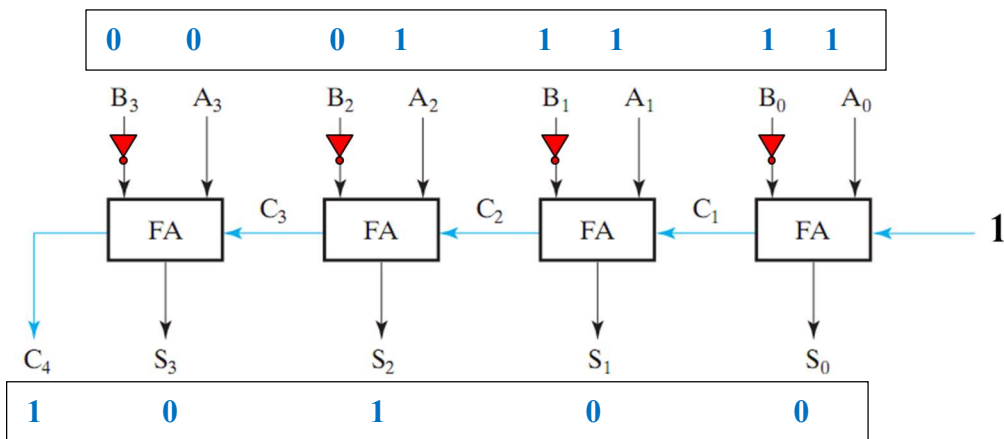- (c) Draw the **4-bit** binary subtractor circuit. Show the **inputs and outputs** of the circuit to compute **(7 - 3)**.



THE END