CSC 220: Computer Organization

Labwork-10

Experiment: Design the 4-bit ALU using Arithmetic and Logic Units